

11/06/2007

6.01

①

Today




- 1) Fun With Op-amps
- 2) Op-amp Nonidealities
- 3) (If Time) Head Controller model

Announcements

- 1) Hand In Lab
- 2) Midterm Rules
 - Start on Thursday Lab today
 - Hand in Work on Thursday
 - Finish Lab on Thursday
 - Serious about Checkoffs

(2)

Op-amp

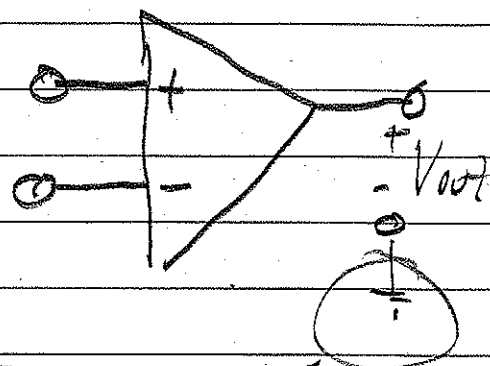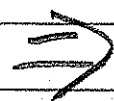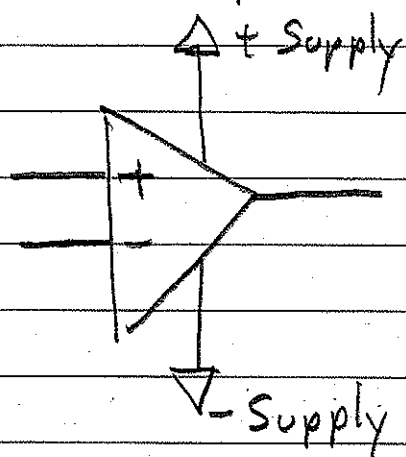


Halfway
between + Supply &
- Supply

Design Rule

If the op-amp is connected "correctly":
1) Then the output will adjust so $V_+ = V_-$
2) the current entering V_+ & V_- is zero

Inverting Amp (Output feeds back to V_-)

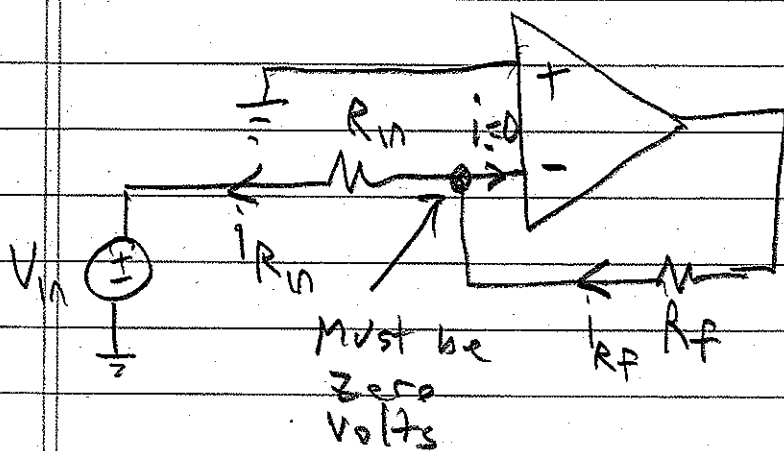

$$i_{R_{in}} = i_{R_f}$$

$$\frac{0 - V_{in}}{R_{in}} = \frac{V_{out} - 0}{R_f}$$


$$\frac{V_{out}}{V_{in}} = - \frac{R_f}{R_{in}}$$

"Virtual ground"

3


Non-Inverting

(Output feeds back to V_-)

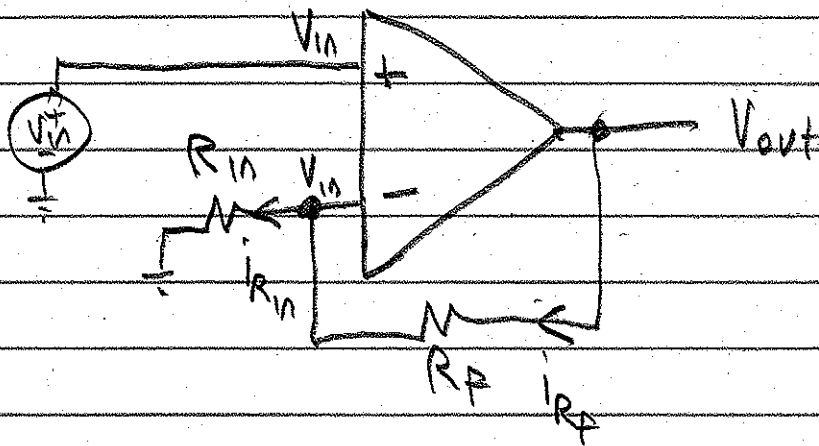

$$\begin{aligned} i_{R_F} &= i_{R_{in}} \\ \frac{V_{out} - V_{in}}{R_F} &= \frac{V_{in} - 0}{R_{in}} \\ \frac{V_{out}}{V_{in}} &= \left(1 + \frac{R_F}{R_{in}}\right) \end{aligned}$$

Super position Works

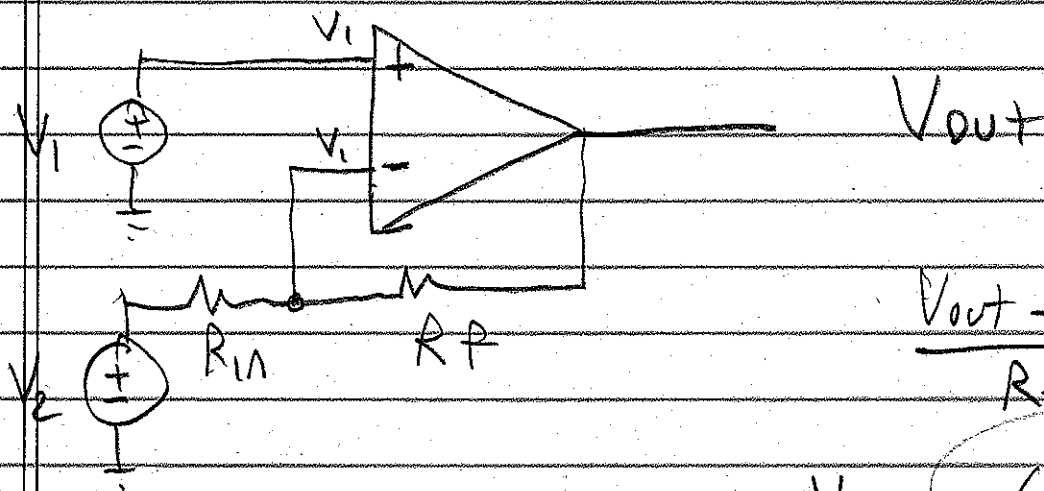

$$\frac{V_{out} - V_1}{R_F} = \frac{V_1 - V_2}{R_{in}}$$



$$V_{out} = \left(1 + \frac{R_F}{R_{in}}\right) V_1 - \frac{R_F}{R_{in}} V_2$$

Result
assuming
 $V_2 = 0$


Result
assuming
 $V_1 = 0$

④

Level Shifting

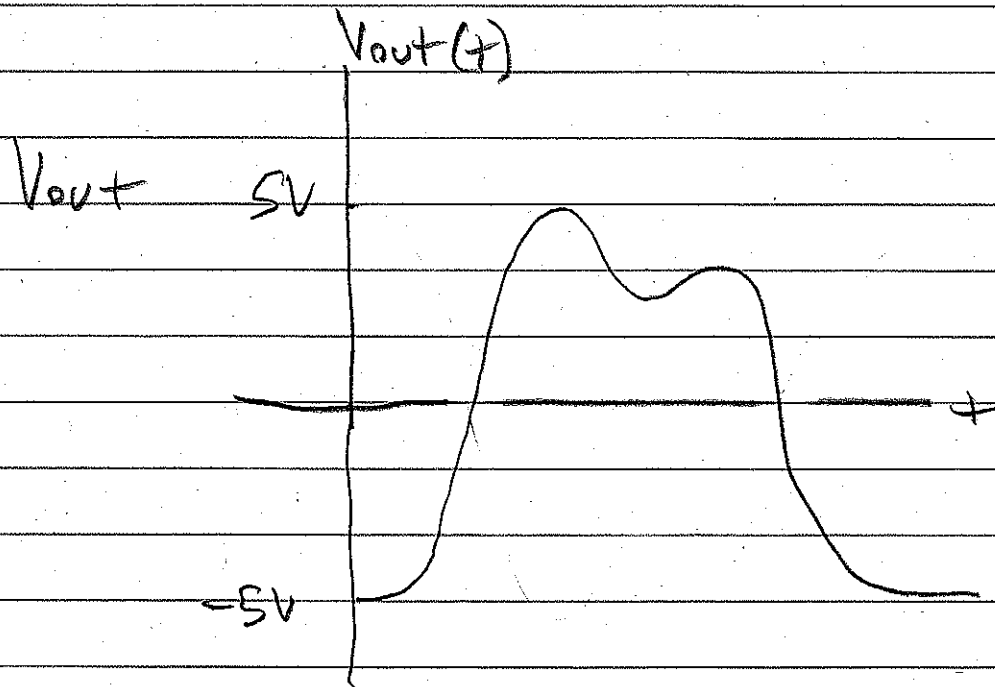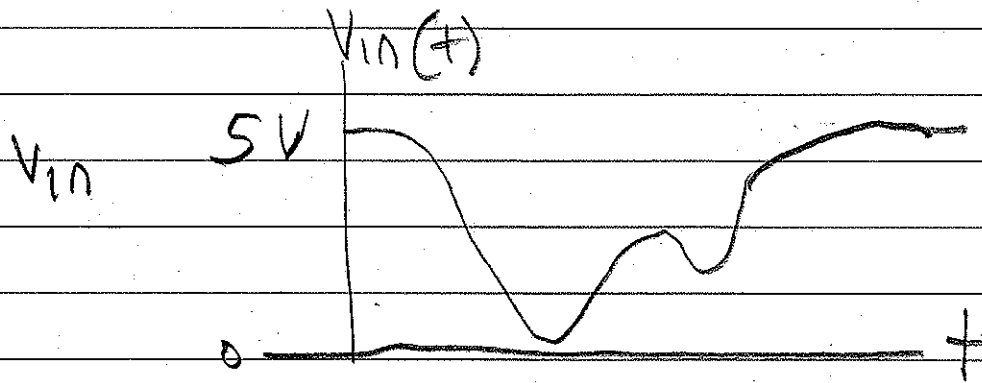
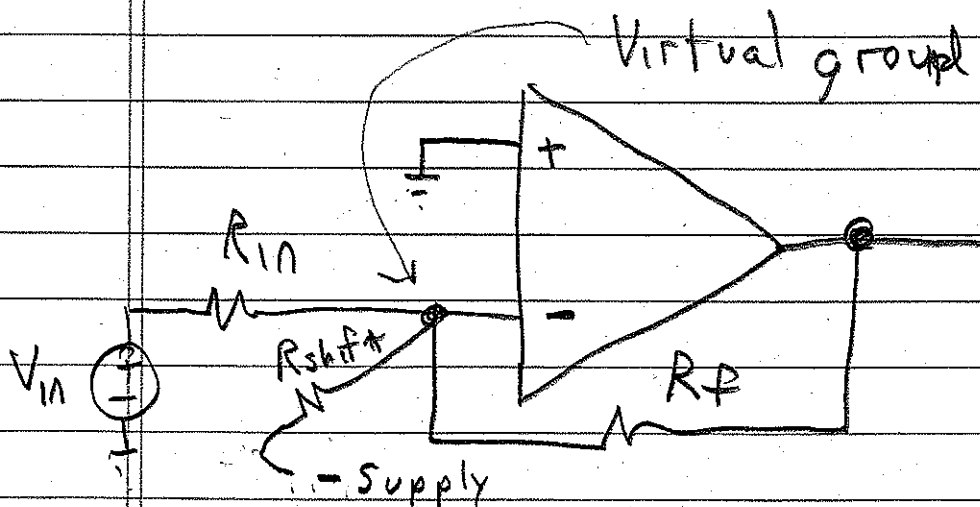
$$V_{out} = -2 * V_{in} + 5 \leftarrow \text{Level Shift}$$



5



Super position to the Rescue

$$V_{out} = -2 * V_{in} + 5$$

assuming
-Supply
to R_{shift}
= 0


assuming
 $V_{in} = 0$
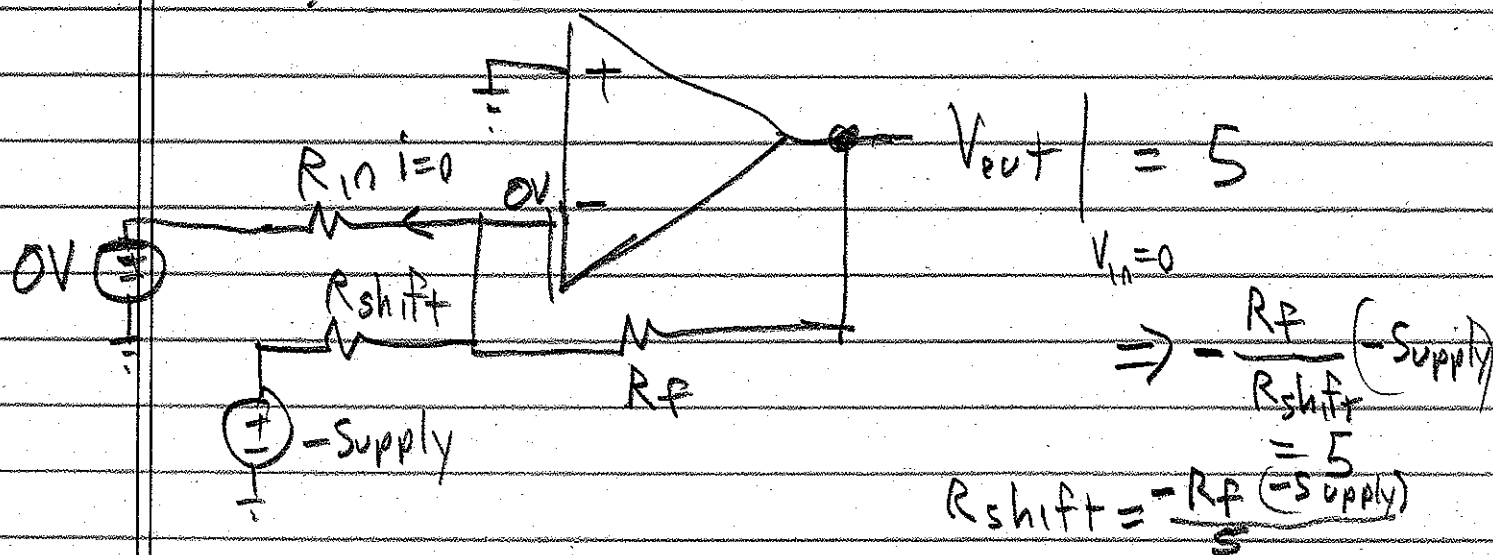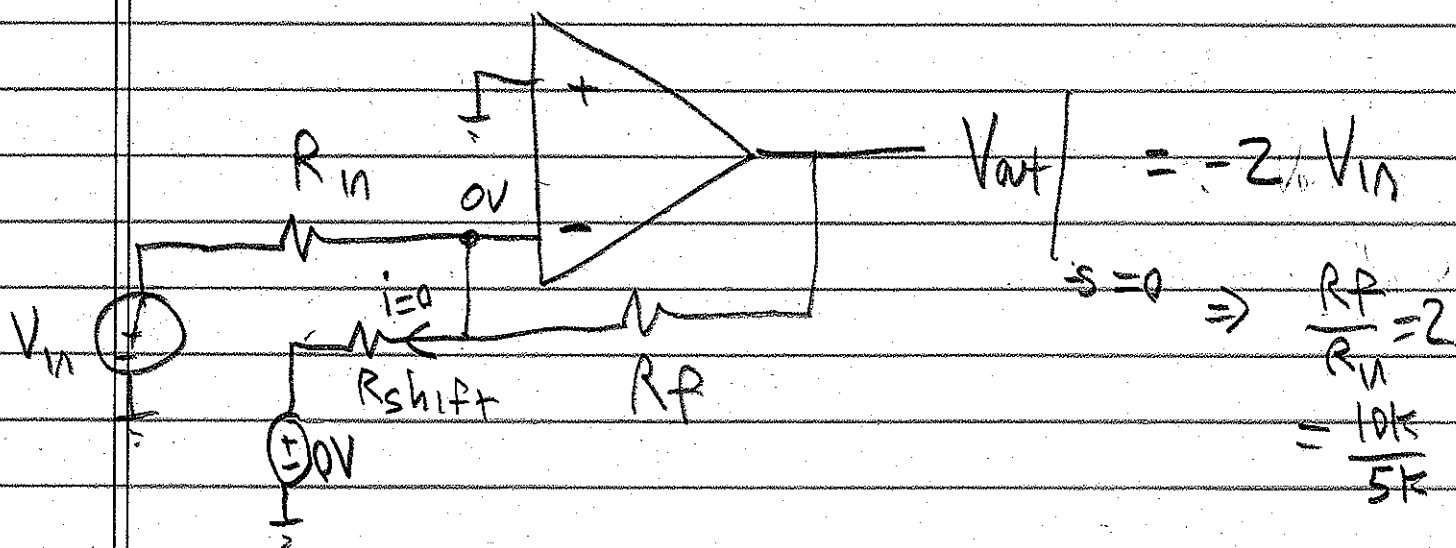
$$\Rightarrow \frac{R_f}{R_{in}} = 2 \quad \text{e.g.} \quad \frac{R_f = 10k}{R_{in} = 5k}$$



6


Use an op-amp Follower

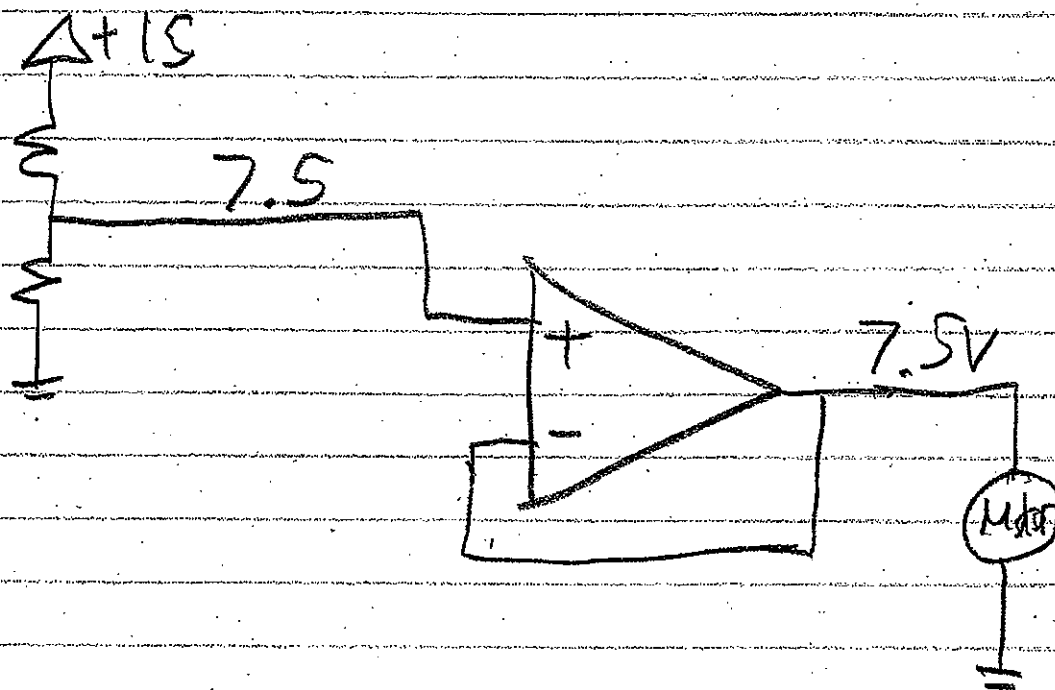

Why does follower help?


Need a better Model of op-amp!

More Detailed Op-amp Model

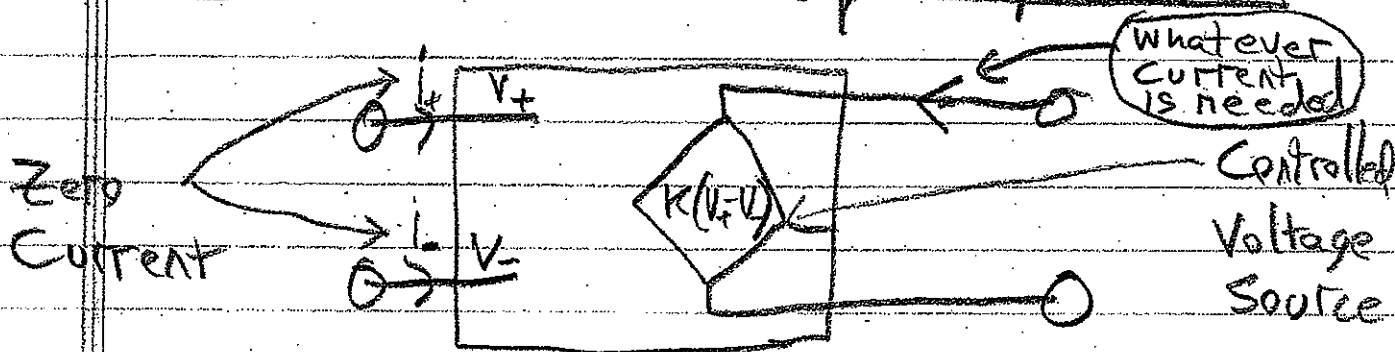

7

Follower

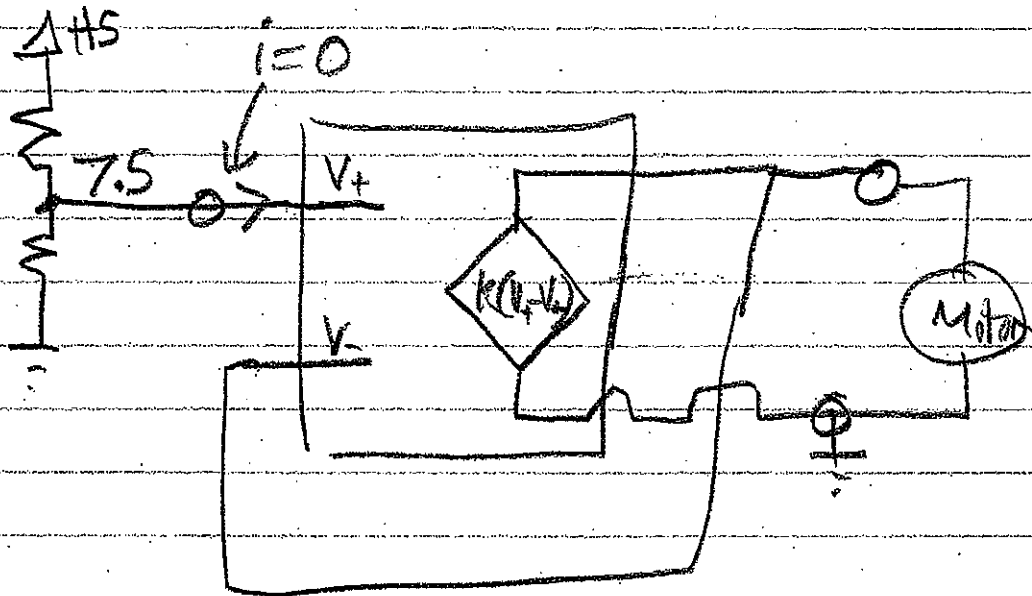

$$V_o = K (V_+ - V_-)$$


$\nwarrow = V_o$

≈ 1 for large K

$$V_o = K (7.5 - V_o) \Rightarrow V_o = \frac{K}{K+1} 7.5$$

8

Non-Inverting Amp Using Detailed Model

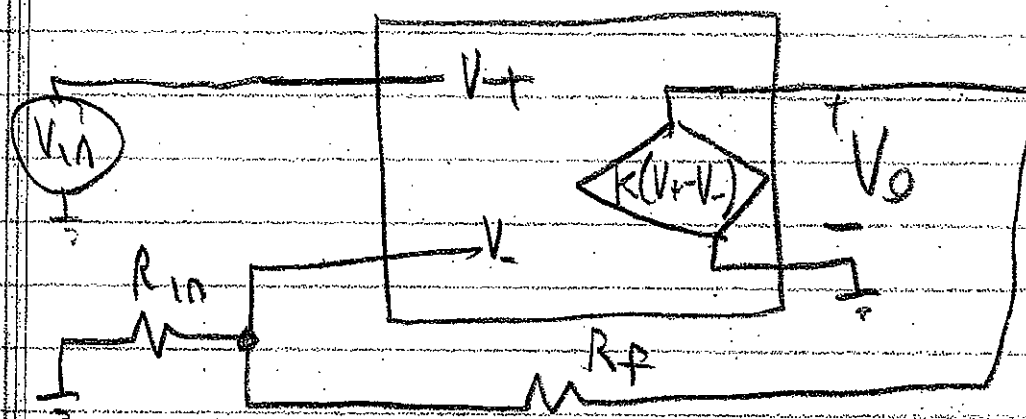

$$V_o = K (V_+ - V_-)$$

$\uparrow = V_o \frac{R_{in}}{R_{in} + R_f}$

$$V_o = K \left(V_{in} - \left(\frac{R_{in}}{R_{in} + R_f} \right) V_o \right)$$

$$\left(1 + K \frac{R_{in}}{R_{in} + R_f} \right) V_o = K V_{in}$$


$$V_o = \frac{K}{1 + K \frac{R_{in}}{R_{in} + R_f}} V_{in}$$

$= 1 + \frac{R_f}{R_{in}} \text{ if } K \text{ large}$


9

Question About Followers

"Good" Follower

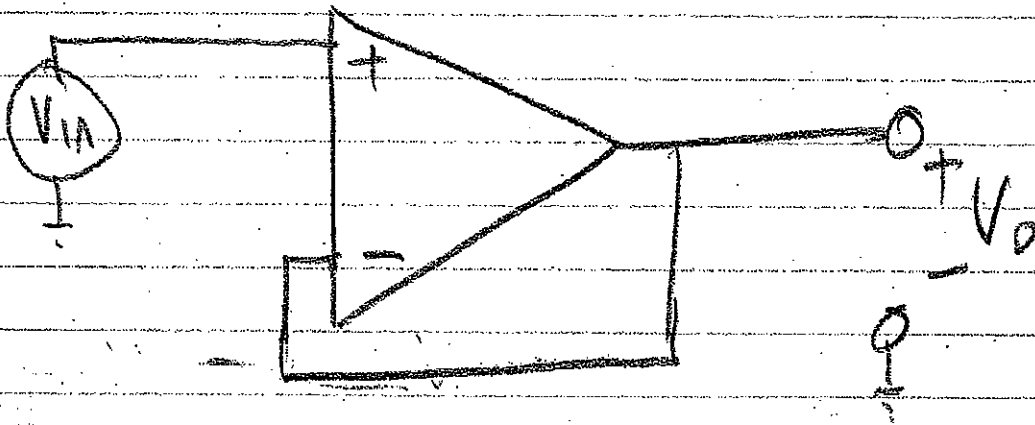


"Bad" Follower

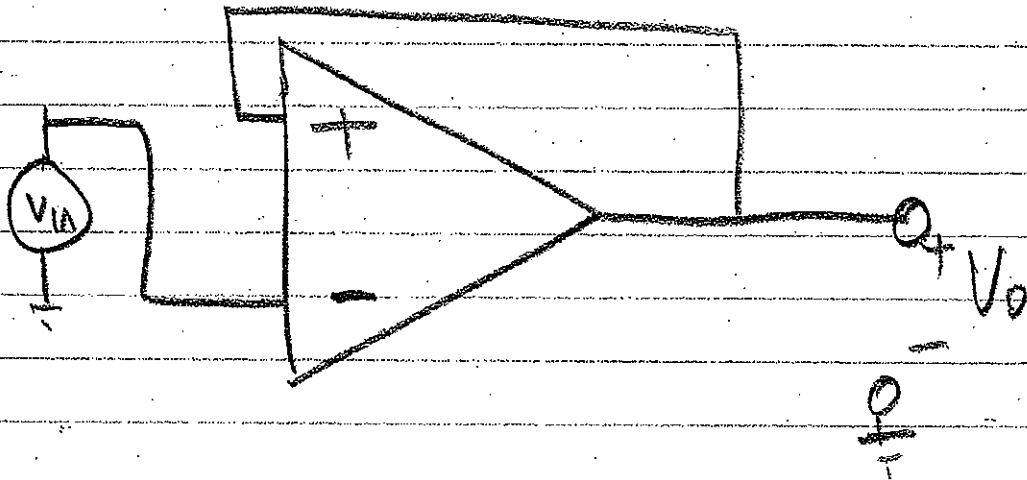


10

Simple Model

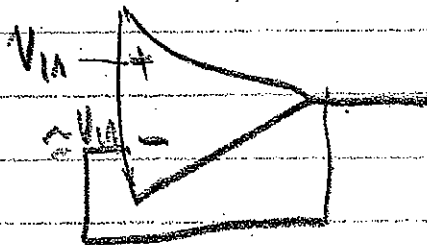

V_o

$$V_o \approx V_{in}$$

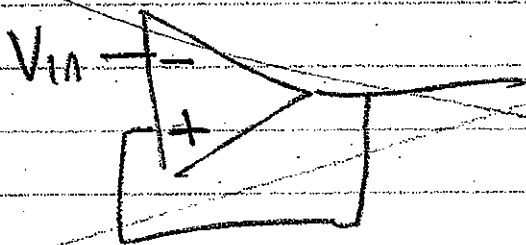


V_o

$$V_o \approx V_{in}$$

Wrong

More Detailed Model does not help

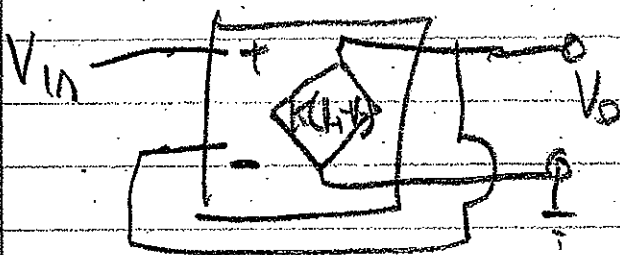


$$V_o = K(V_+ - V_-)$$

$V_+ = V_{in}$
 $V_- = V_o$

Wrong

$$V_o = \frac{K}{K+1} V_{in} \approx \frac{K}{K+1} V_{in}$$

$K \text{ large}$

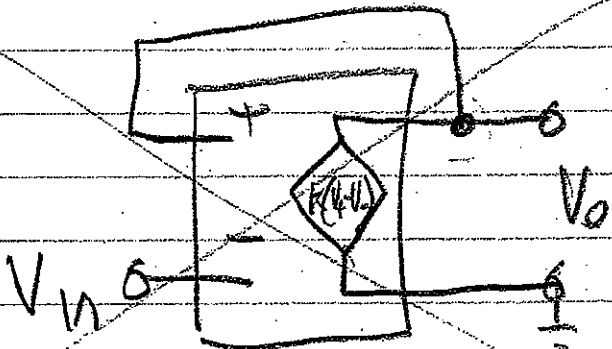

$$V_o = K(V_+ - V_-)$$

$V_+ = 0$
 $V_- = V_o$



$$(1-K)V_o = -KV_{in}$$

$$V_o = \frac{K}{K-1} V_{in} \approx V_{in}$$

(11)

More Detailed Op amp model

What to Model

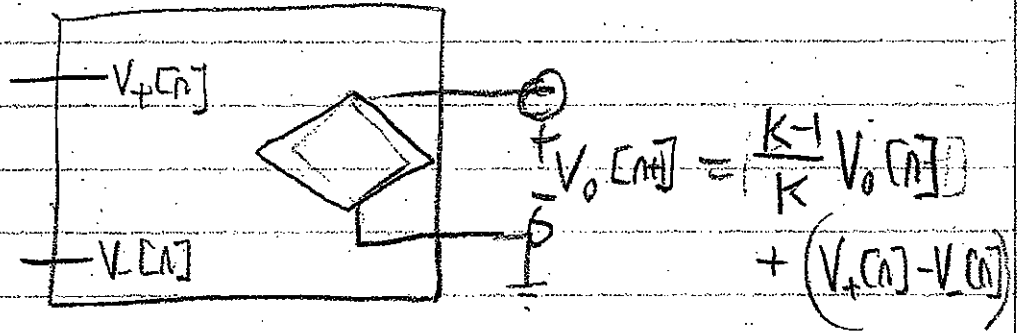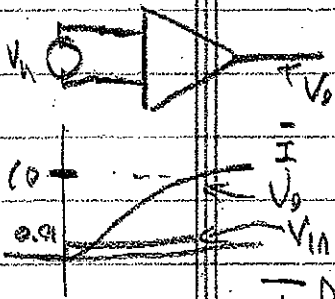If \$K = 1000\$

$$V_o[n] = \frac{999}{1000} V_o[n] + (V_+[n] - V_-[n])$$

What if \$V_+[n] - V_-[n] = 0.1 \forall n\$If \$V_o[0] = 0\$

$$V_o[n] = \sum_{k=0}^{n-1} \left(\frac{999}{1000} \right)^{(n-1-k)} (V_+[k] - V_-[k])$$

$$V[1] = (V_+[0] - V_-[0])$$

$$V[2] = \frac{999}{1000} (V_+[0] - V_-[0]) + (V_+[1] - V_-[1])$$

(12)

Eventually


$$V_o[n] = V_o[n-1] = V_o^* \text{ (for large } n)$$

$$V_o^* - \frac{999}{1000} V_o^* = 0.01$$

$$= \frac{1}{1000} V_o^* = 0.01$$

$$V_o^* = 1000$$

Now Back to the question

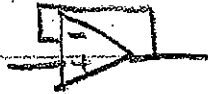

$$V_o[n] = \frac{999}{1000} V_o[n-1] + (V_+[n-1] - V_o[n-1])$$

$$V_o[n] = -\frac{1}{1000} V_o[n-1] + V_+[n-1]$$

Not freq < 1




$$V_o[n] = \frac{999}{1000} V_o[n-1] + (V_+[n-1] - V_o[n-1])$$

$$V_o[n] = \frac{1.999}{1000} V_o[n-1] - V_+[n-1]$$

Not freq > 1

Robot Head Controller

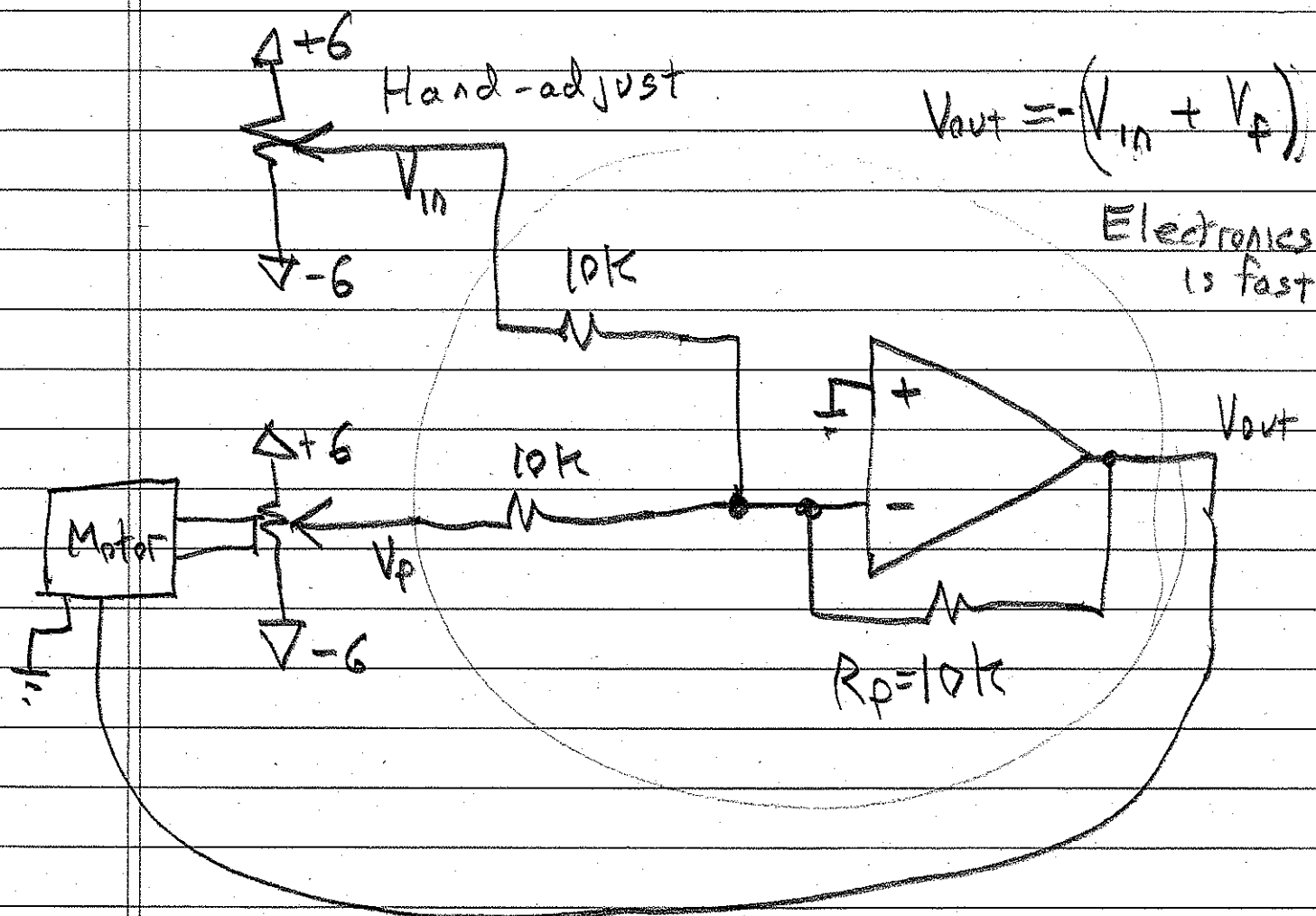

Motor Model

$$V_f(n) = f(V_{out}(n), V_{out}(n-1), V_{out}(n-2))$$

What we know Voltage across Motor \rightarrow Speed

Very Simple

$$\left\{ \underbrace{\frac{V_F(n) - V_F(n-1)}{\Delta t}}_{\text{Motor Speed}} = \underbrace{K_1}_{?} V_{out}(n-1) \right.$$

$$V_F(n) = V_F(n-1) + \Delta t K_1 V_{out}(n-1)$$

$$V_F(n) = V_F(n-1) + (K_1 \Delta t) (-V_{in}(n-1) + V_F(n-1))$$

$$V_F(n) = \underbrace{(1 - K_1 \Delta t)}_{\text{Natural frequency}} V_F(n-1) - K_1 \Delta t V_{in}(n-1)$$

Natural
frequency

What happens if we swap leads?