

6.01


10/30/2007

①

Today


- 1) Using Thevenin Equivalents
- 2) Making Circuits Input/Output
- 3) Op-Amps
- 4) Basic Op-Amp Circuits

Example Problem

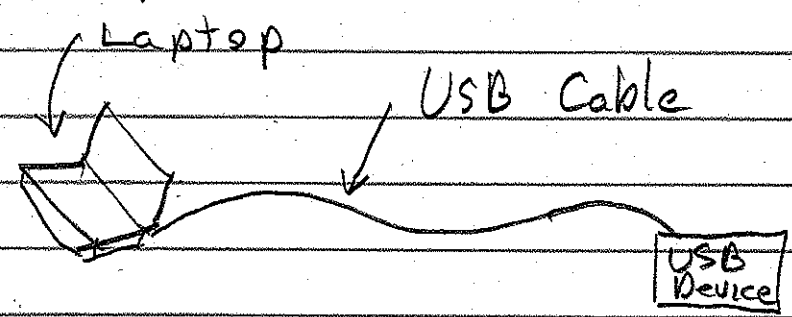


Question How big a load can USB drive? Does it depend on cable length?

Models

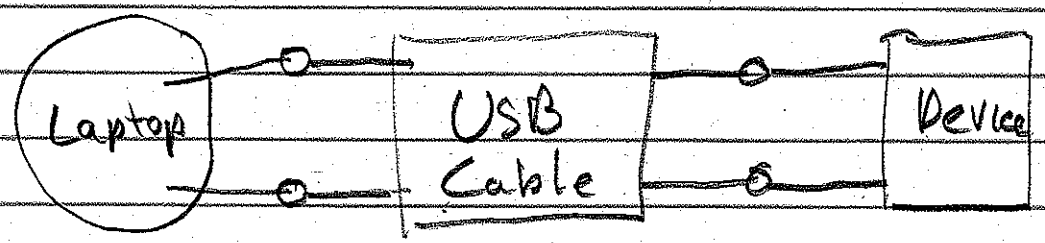

Approximate Model

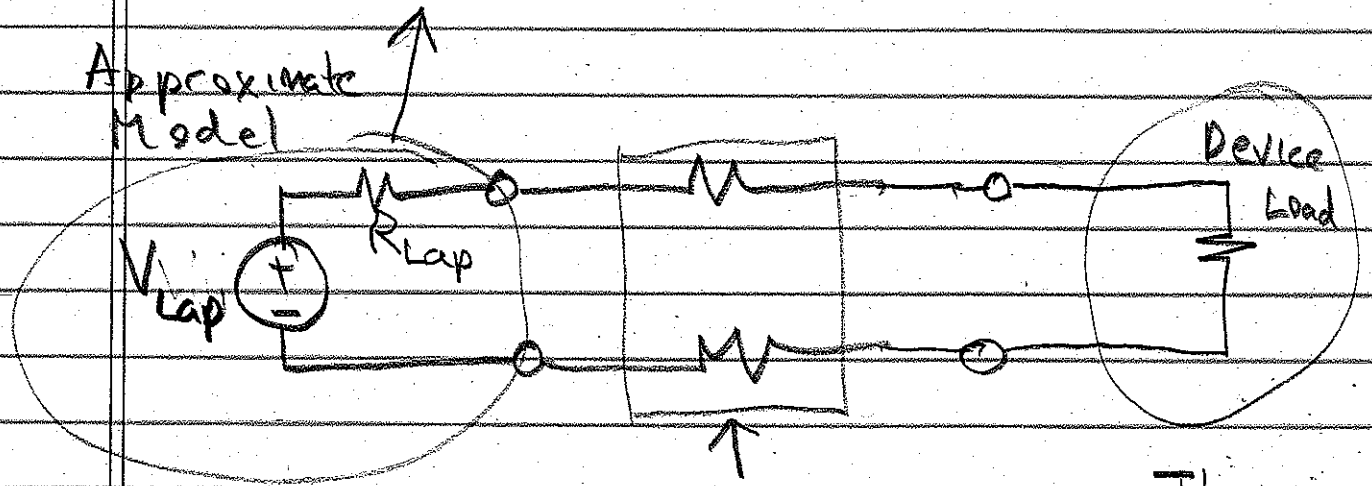

Thevenin Equivalent


Wire Resistance

Thevenin Equivalent?


3

Aside on Thevenin Equivalents

Consider following circuit

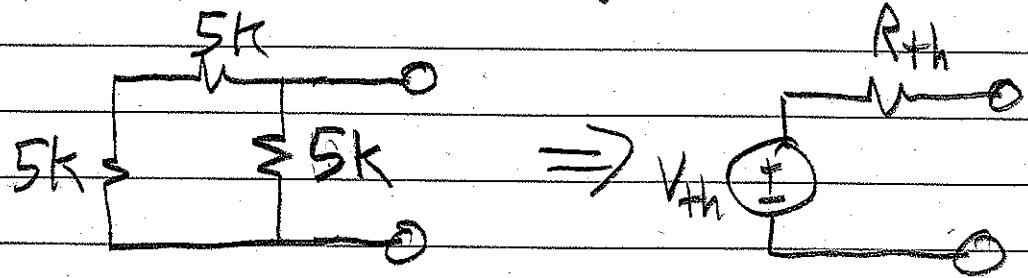

Follow Standard algorithm

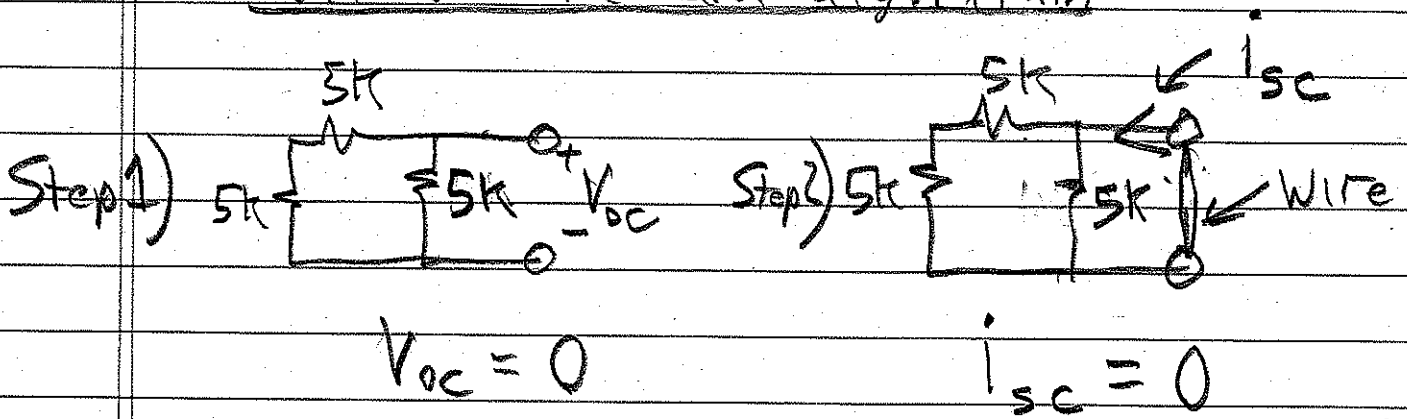

$$V_{oc} = 0$$


$$i_{sc} = 0$$

$$V_{th} = 0$$

$$R_{th} = \frac{V_{th}}{i_{sc}} = ?$$



Method Fails!

But

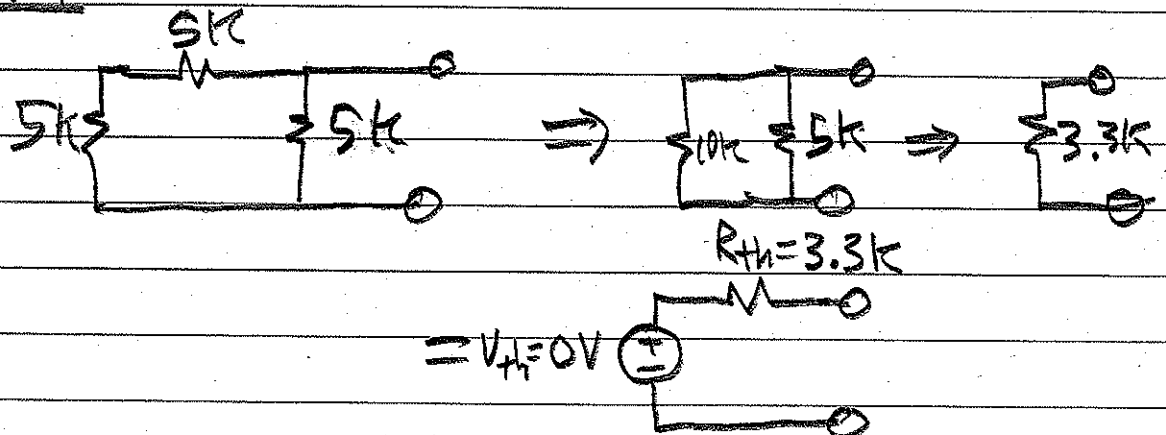

④

Back to USB problem

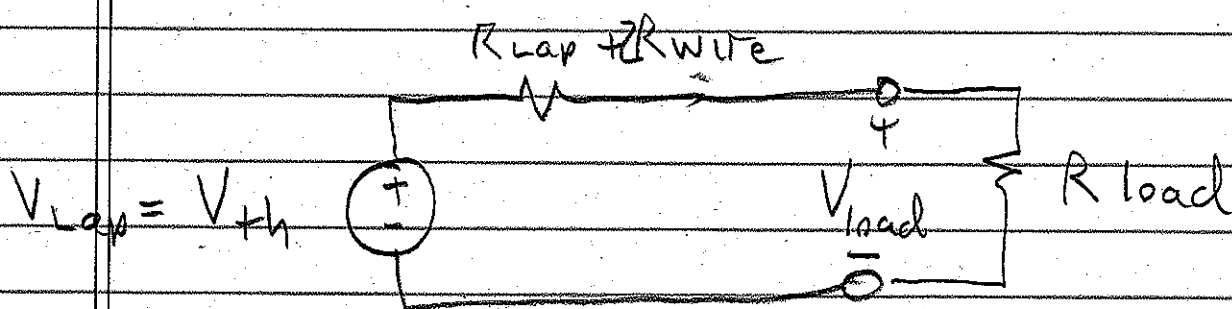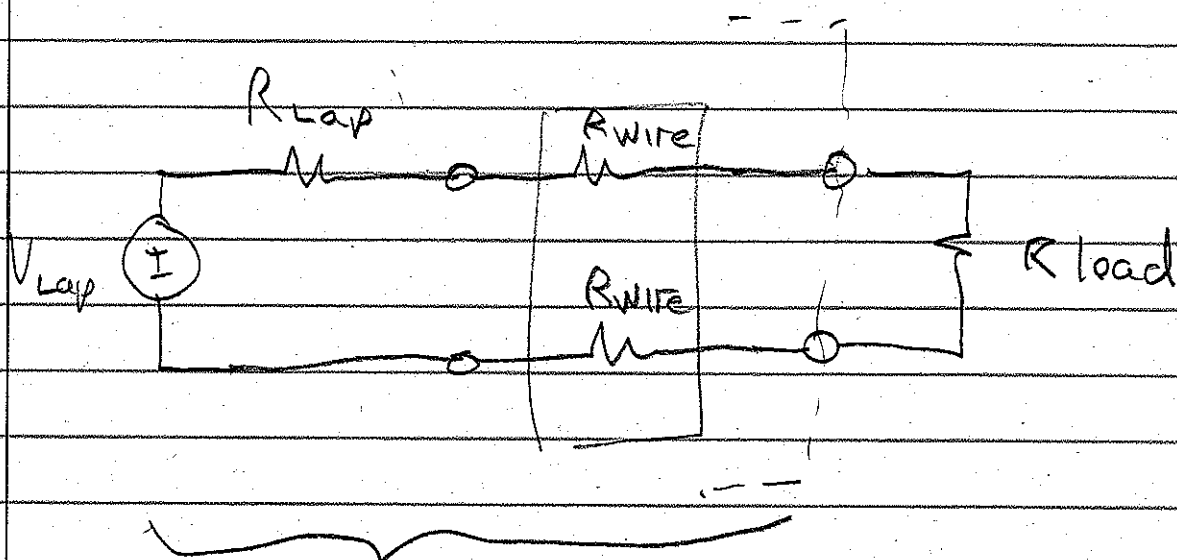

$$V_{load} = \frac{R_{load}}{R_{load} + R_{Lap} + 2 R_{wire}} V_{Lap}$$

Device Works if $V_{Lap} = 5V$

V_{load} is with 10% of V_{Lap}

$$\Rightarrow \frac{R_{load}}{R_{load} + R_{Lap} + 2 R_{wire}} > 0.9$$

(5)

Short Cable Case

$$R_{\text{lap}} = 50\Omega \quad R_{\text{wire}} = 5\Omega$$

Minimum R_{load} ?

$$\frac{R_{\text{load}}}{R_{\text{load}} + 60\Omega} \geq 0.9$$

$$0.1 R_{\text{load}} = 54\Omega \Rightarrow R_{\text{load}} \geq 540\Omega$$

Long Cable Case




$$R_{\text{lap}} = 50\Omega \quad R_{\text{wire}} = 25\Omega$$

$$\frac{R_{\text{load}}}{R_{\text{load}} + 100\Omega} = 0.9$$

$$R_{\text{load}} \geq 900\Omega$$

6

Driving a Motor

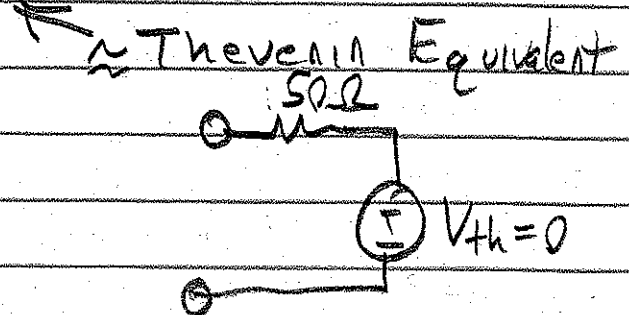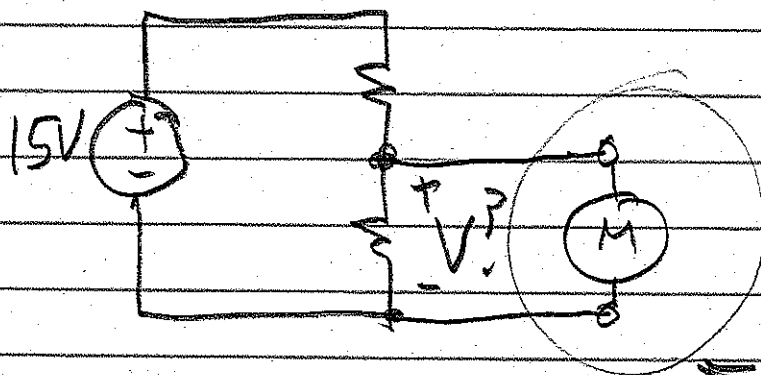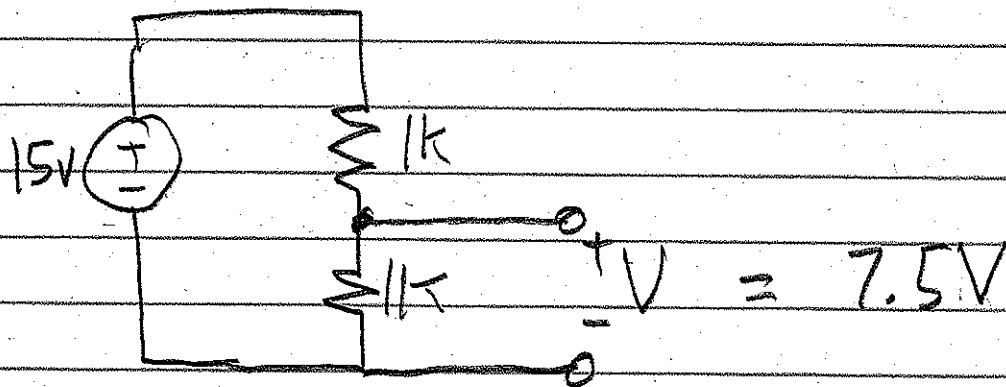

$$\Rightarrow V \approx 0.75V$$

Motor Loaded the Divider

7

Input/Output For Circuits

Suppose

```
def f(x):  
    ~~~~~  
    return z
```

Could you design software if


$$y = f(x_1) + f(x_2)$$

$$z = 3.0 * f(x_1)$$

↓
the
Value
Returned
by f
depends
on how
you
used it

No!

But what about the Divider?

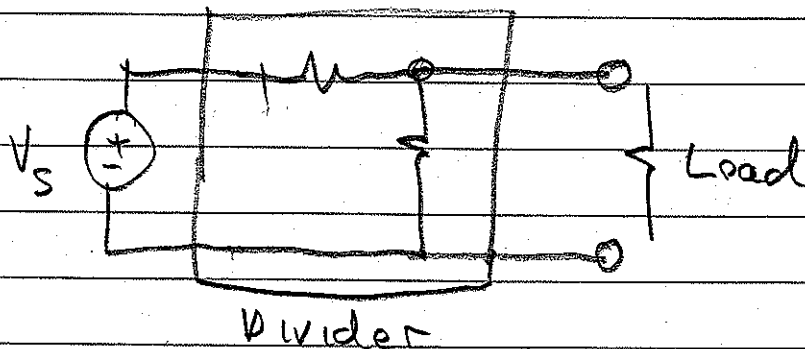


Divider result depends on how you use it!


8

Need a "buffer"

Voltage-Controlled Voltage Source


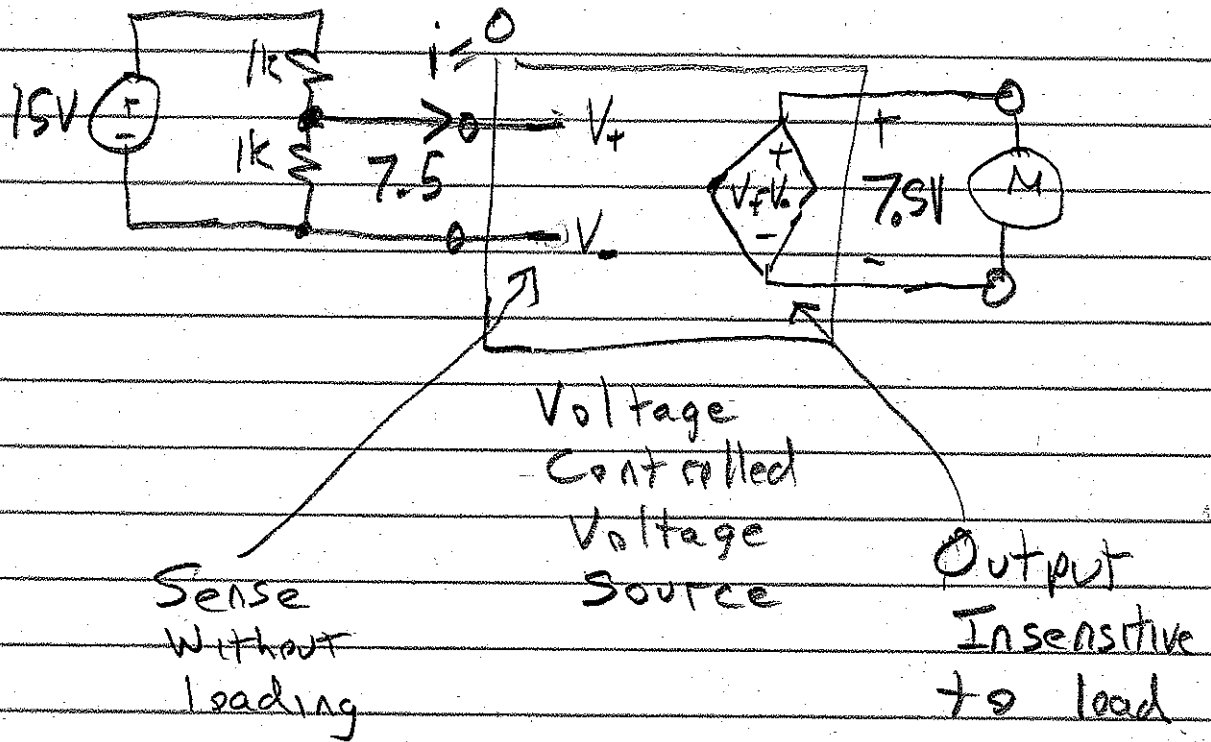


With Buffers

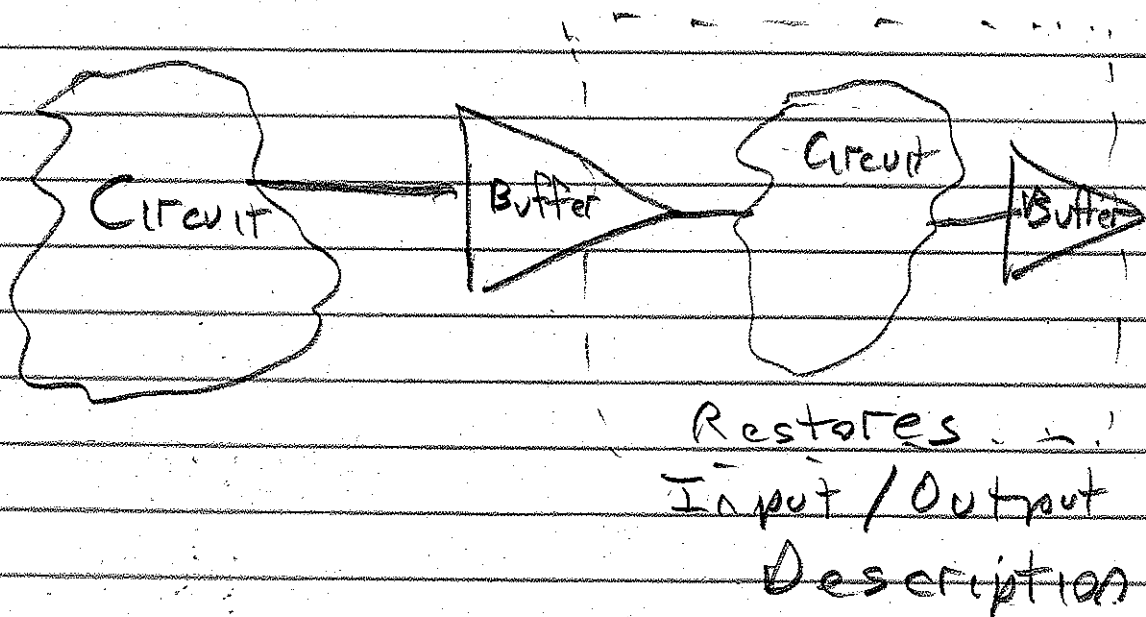


9


The Op - Amp

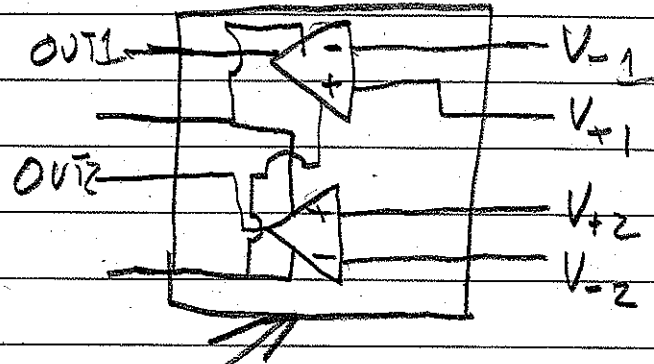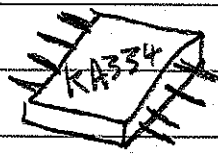


What's inside

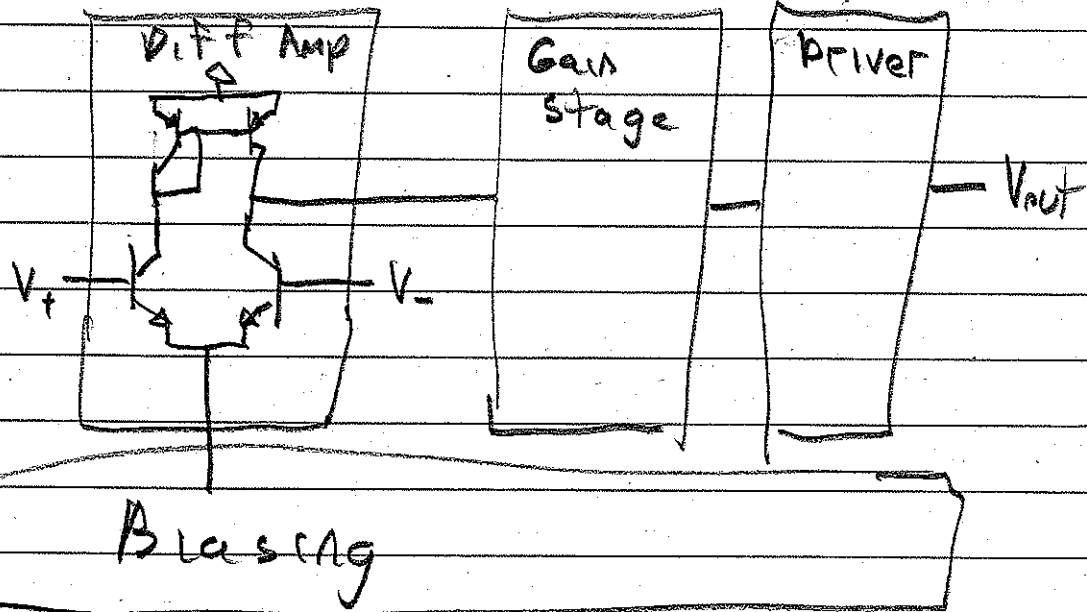

Op - Amp

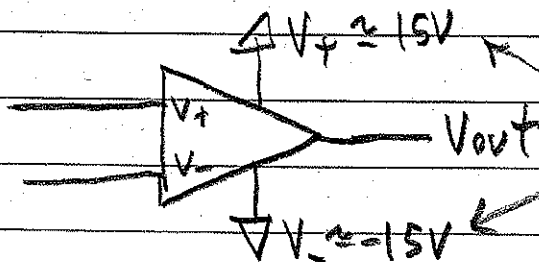


Usual View

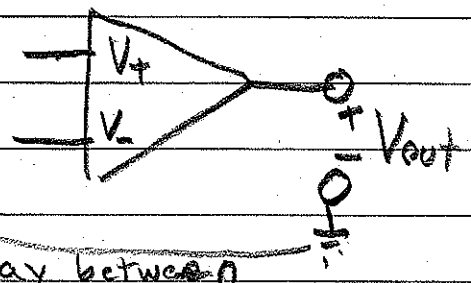

Half way between


(10)

The Op-Amp Model

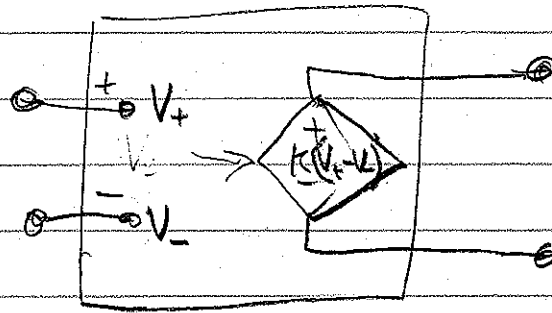

$$K \approx 10,000$$

Simple Case - Buffer

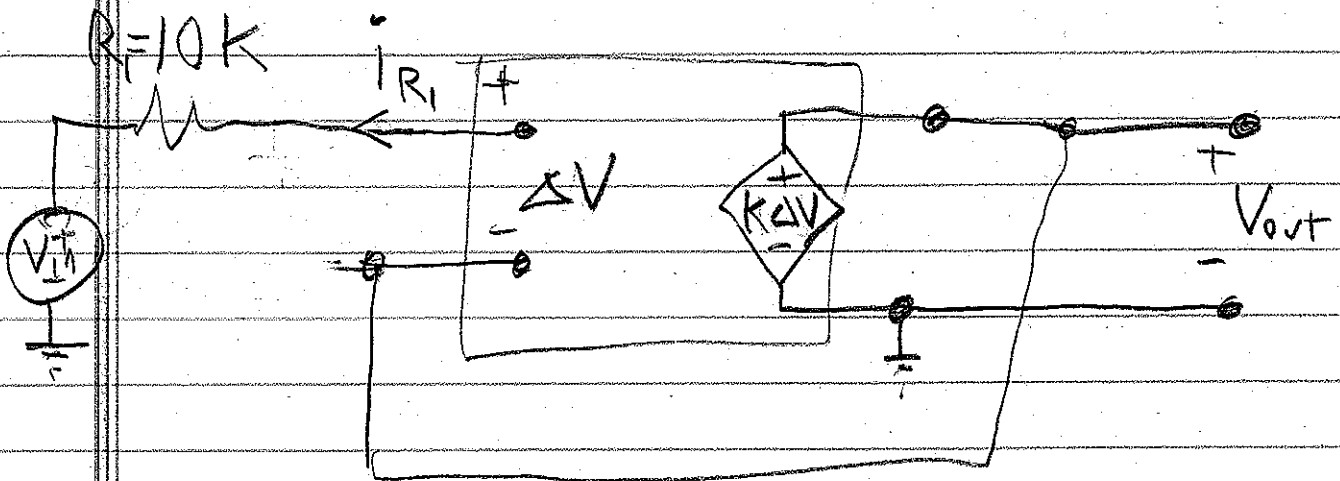

$$\begin{aligned}
 i_{R1} &\approx 0 \Rightarrow V_+ = V_{in} \\
 V_- &= K \Delta V \\
 \Delta V &= (V_+ - V_-) \\
 V_{out} &= K \Delta V
 \end{aligned}
 \left. \vphantom{\begin{aligned} i_{R1} &\approx 0 \Rightarrow V_+ = V_{in} \\ V_- &= K \Delta V \\ \Delta V &= (V_+ - V_-) \\ V_{out} &= K \Delta V \end{aligned}} \right\}
 \begin{aligned}
 \Delta V &= \frac{1}{1+K} V_{in} \\
 V_o &= \frac{K}{1+K} V_{in} \\
 &\approx V_{in}
 \end{aligned}$$


(11)

Simple Model

The output of the op-amp adjusts so as to make the V_+ input and the V_- input nearly equal

* And no current flows into the V_+ and V_- terminals

Simple Circuit Follower

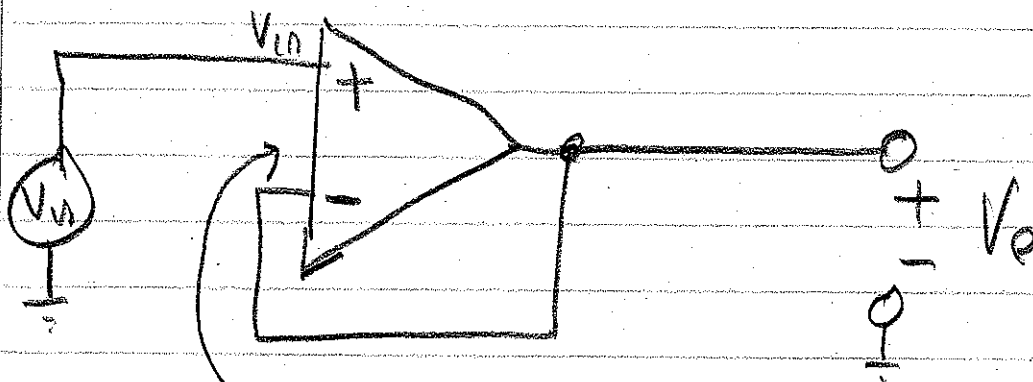


V_o adjusts
to make $V_- = V_{in}$

$$\Rightarrow V_o = V_{in}$$


12

Simple Model is great for Design

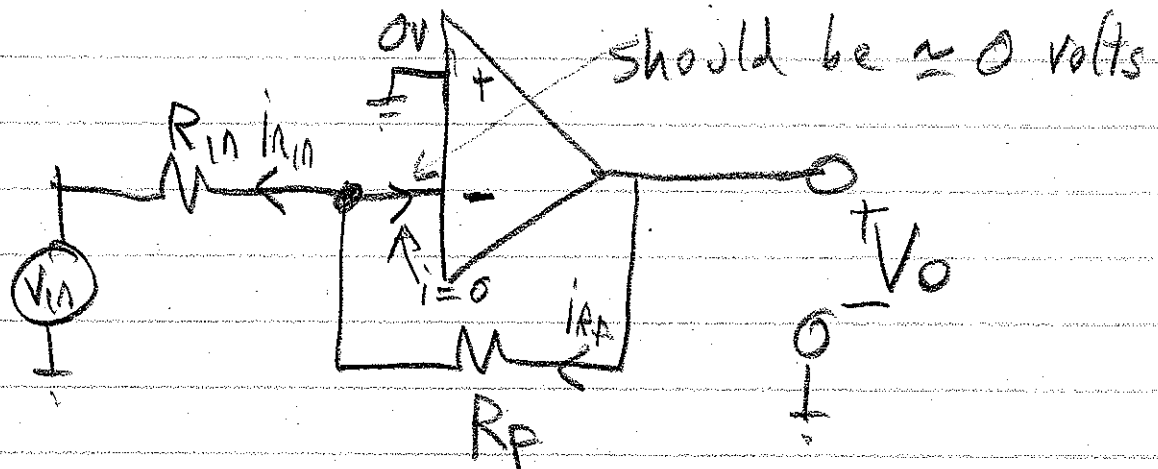

$$\frac{V_o - 0}{R_F} = i_{RF} = i_{R_{in}} = \frac{0 - V_{in}}{R_{in}}$$
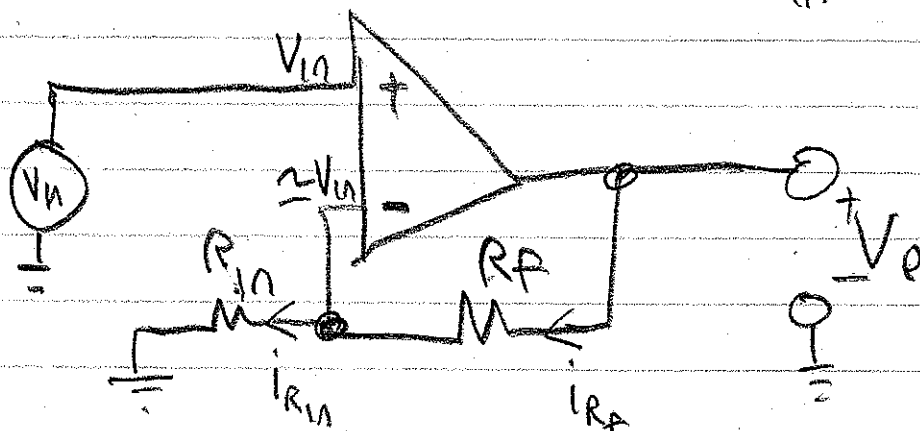
$$\Rightarrow V_o = -\frac{R_F}{R_{in}} V_{in}$$




$$\frac{V_o - V_{in}}{R_F} = \frac{V_{in} - 0}{R_{in}} \Rightarrow V_o = \left(1 + \frac{R_F}{R_{in}}\right) V_{in}$$

13

More Complicated Circuits

Summer (Inverting)

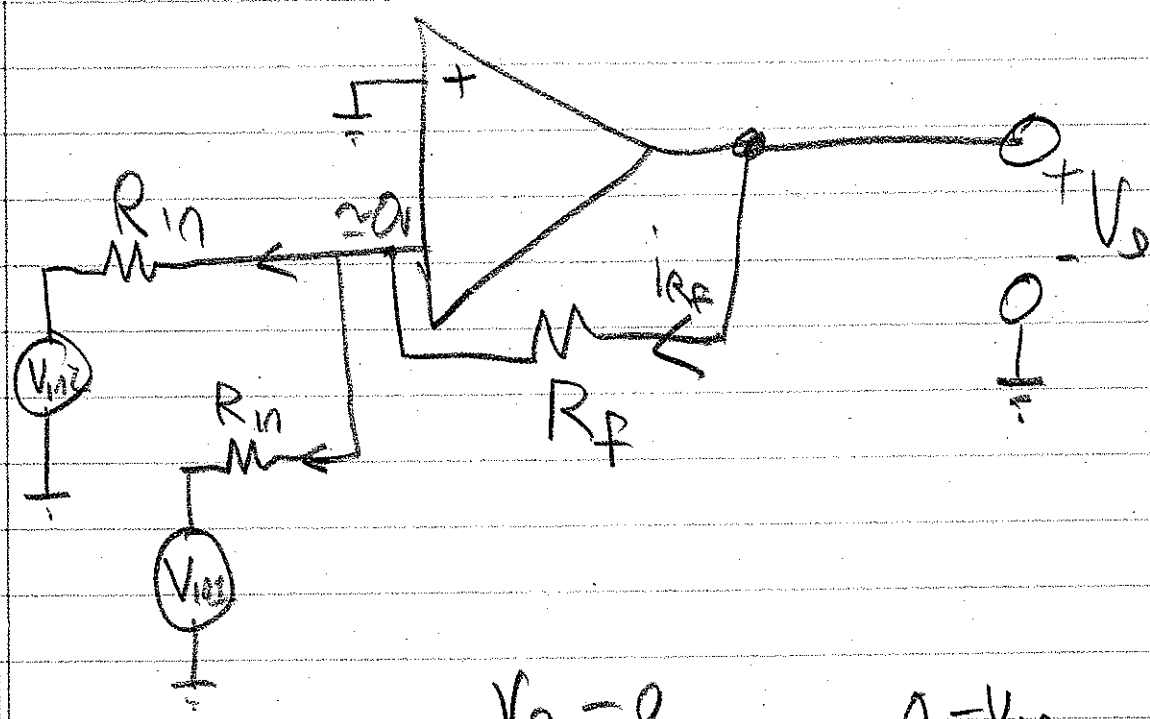

$$\frac{V_o - 0}{R_F} = \frac{0 - V_{in2}}{R_{in}} + \frac{0 - V_{in1}}{R_{in}}$$

$$V_o = - \frac{R_F}{R_{in}} (V_{in1} + V_{in2})$$