

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science
6.01—Introduction to EECS I
Fall Semester, 2007

Quiz 8


Name: Solutions

Athena userid: _____@mit.edu

Question 1: For the circuit below, suppose you know the current $i_s = -0.5$ amps, $V_S = 5$ volts and that $R_1 = 2 * R_2$. Please determine numerical values for R_1 and R_2 . Try to use simplifications, you will find it too time-consuming otherwise.

$$R_1 = 30$$

$$R_2 = 15$$

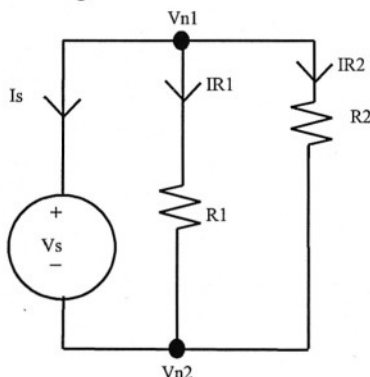

$$i_s = -0.5 = i_{R_1} + i_{R_2}$$


$$R_1 || R_2 = 2R_2 || R_2$$

$$= \frac{2}{3} R_2$$

$$\frac{V_S}{\frac{2}{3} R_2} = 0.5 \Rightarrow \frac{5}{\frac{1}{3}} = R_2$$

$$R_2 = 15$$

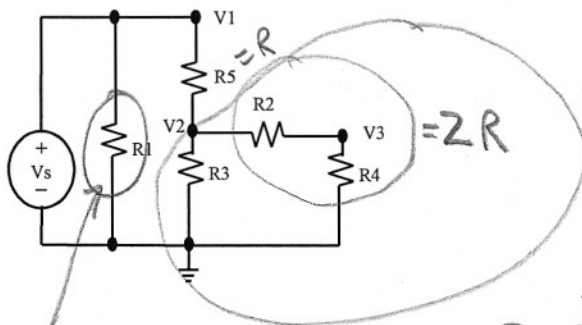Question 2: In the circuit below, suppose $V_S = 5$ volts and all the resistors are equal, that is, $R_1 = R_2 = R_3 = R_4 = R_5$. Please determine the numerical value for V_2 with respect to the ground. Hint: Note that there are series-parallel combinations that you can use to simplify the problem.



Does
Not
affect
 V_2

$$2R || R = \frac{2}{3} R$$

$$V_2 = 5 \cdot \frac{\frac{2}{3} R}{\frac{2}{3} R + R} = 5 \cdot \frac{\frac{2}{3}}{\frac{2}{3} + 1} = 2$$

Voltage Divider