


6.01 10/16/07

①


In Python:

on slides
too much
Front end

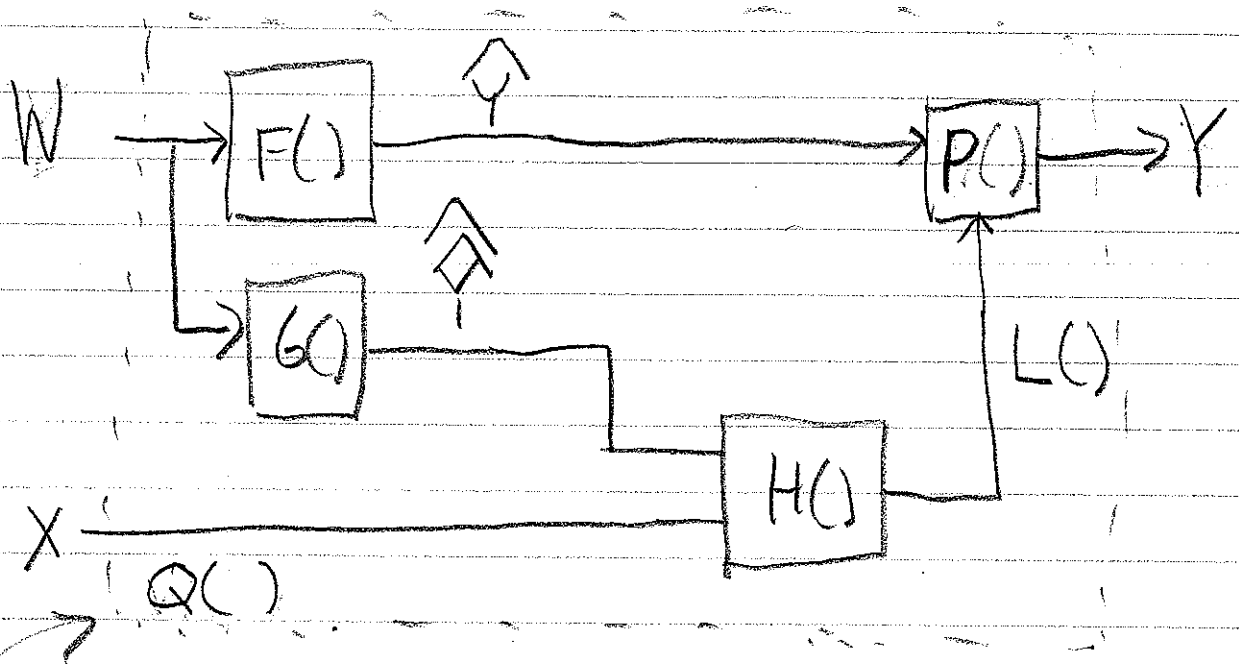Create systems with complex behavior by composing functions which consume inputs to generate outputs



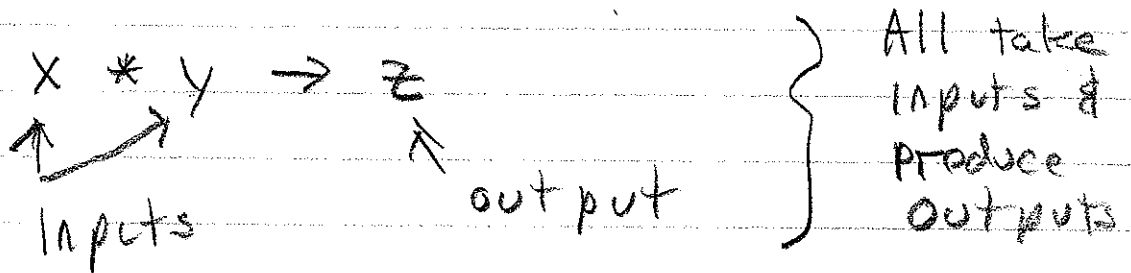Procedures, Class member functions, assignment, *, +, -, %



Hide detail by Abstraction Hierarchy (API)

$$Q(W, X) \rightarrow Y$$


②

Difference Equation Systems Are also Input-output Descriptions

$$\sum a_k W[n+k] = \sum b_l \overset{\text{input}}{X[n+l]}$$

$$\sum c_k V[n+k] = \sum d_l W[n+l]$$


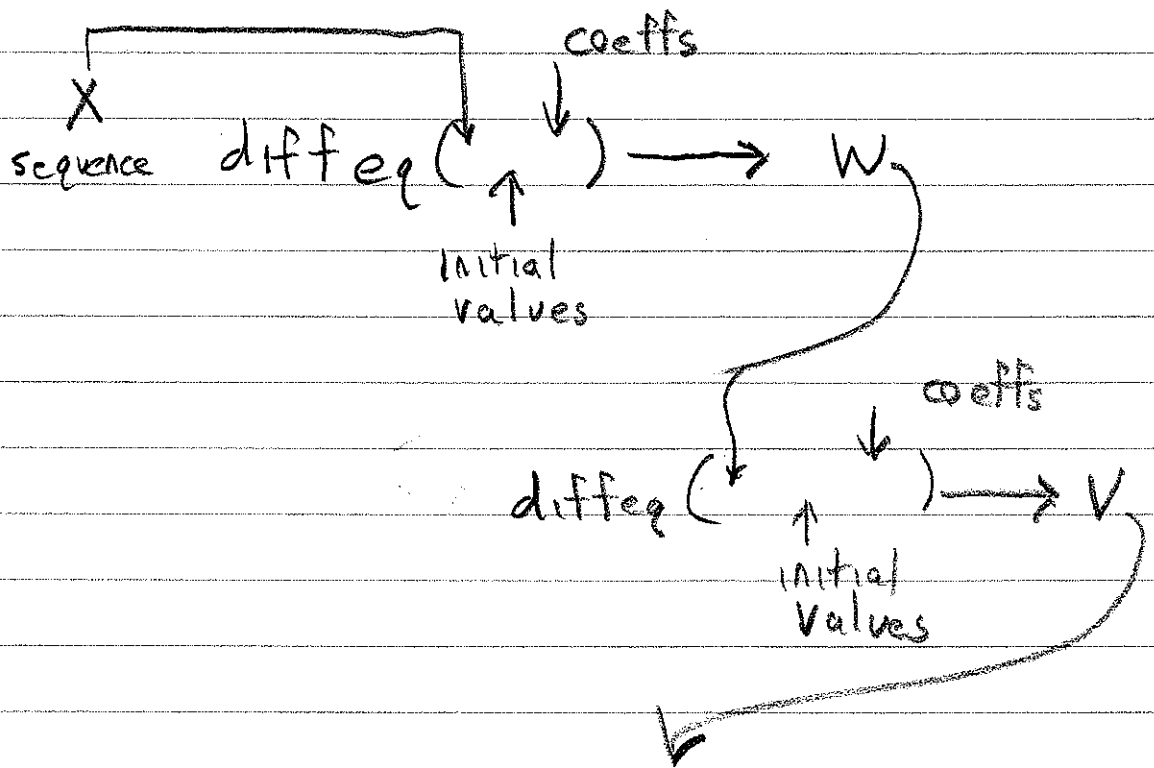
$$\sum f_k \underbrace{Y[n+k]}_{\text{final output}} = \sum g_l V[n+l]$$




All take inputs and produce outputs { + , - , difference equations, scaling

3

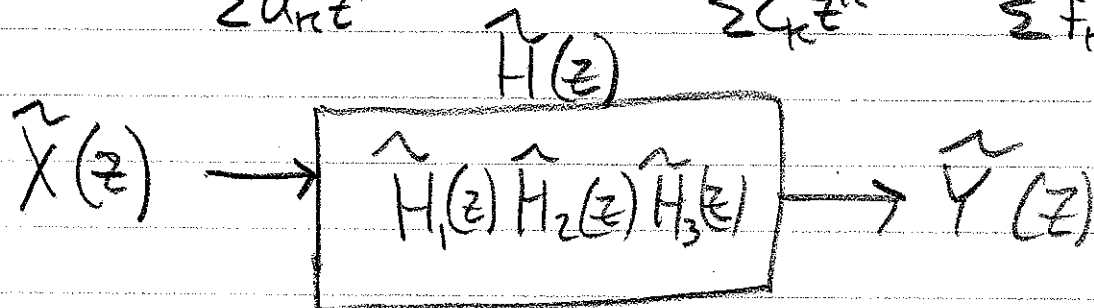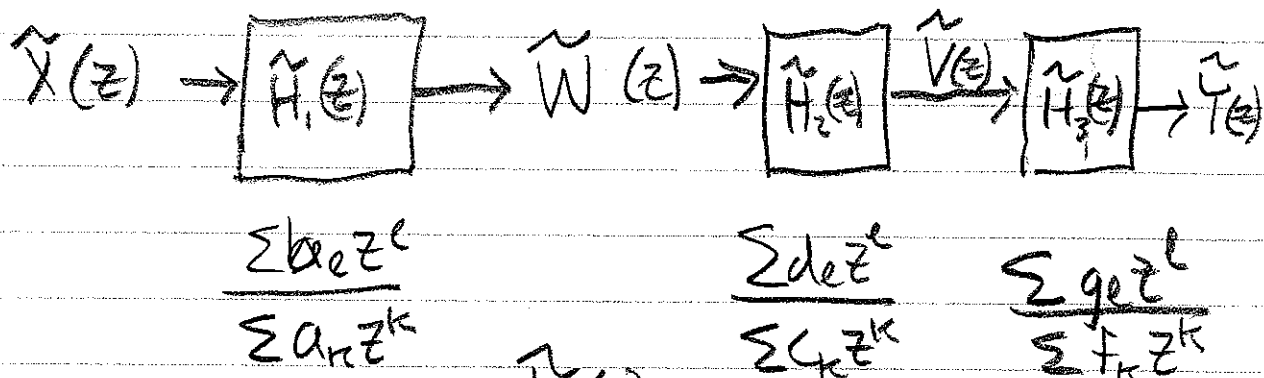Introduced an Analysis Tool z - transform


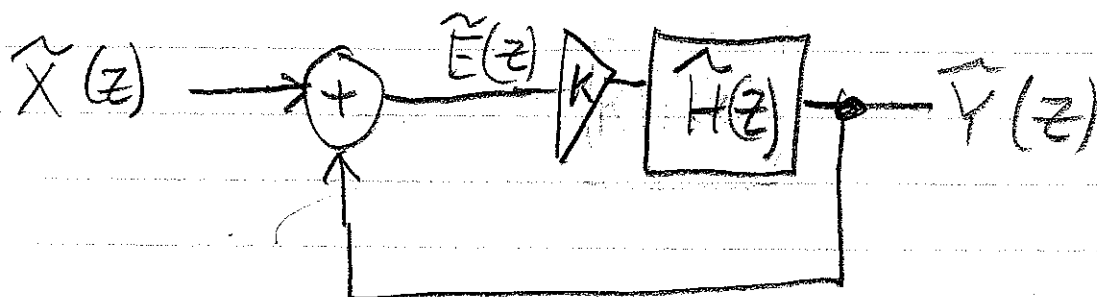
$$\frac{(\sum b_l z^l) (\sum d_l z^l) (\sum g_l z^l)}{(\sum a_k z^k) (\sum c_k z^k) (\sum f_k z^k)}$$




Python $X \rightarrow Y$ simple by design

Diff Eq $X \rightarrow Y$ complicated model \rightarrow need tools
Both Input / Output Views!

④

Input/Output is a limiting perspective

Unidirectional in Nature

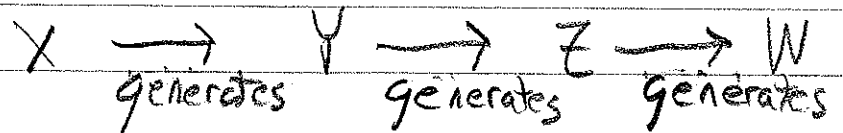

Ex

```
def f(x):
    return x**z
```

$y = f(x)$ Set x then get y

Ex

$$y(n+1) - y(n) = x(n+1) + x(n)$$

$$\tilde{Y}(z) = \left(\frac{z+1}{z-1} \right) \tilde{X}(z)$$

Set $x(n)$ and $y(0)$
then get $y(n)$

Spase Feedback

$$e(n) = k(y_d(n) - y(n))$$

$$\tilde{Y}(z) = \frac{z+1}{z-1} \tilde{C}(z) = \frac{z+1}{z-1} K (\tilde{Y}_d(z) - \tilde{Y}(z))$$


$$\tilde{Y}(z) = \frac{K}{1+K} \tilde{Y}_d(z)$$

Still Unidirectional

→ Set $y_d(n)$
→ get $y(n)$

5


Consider a set of Springs

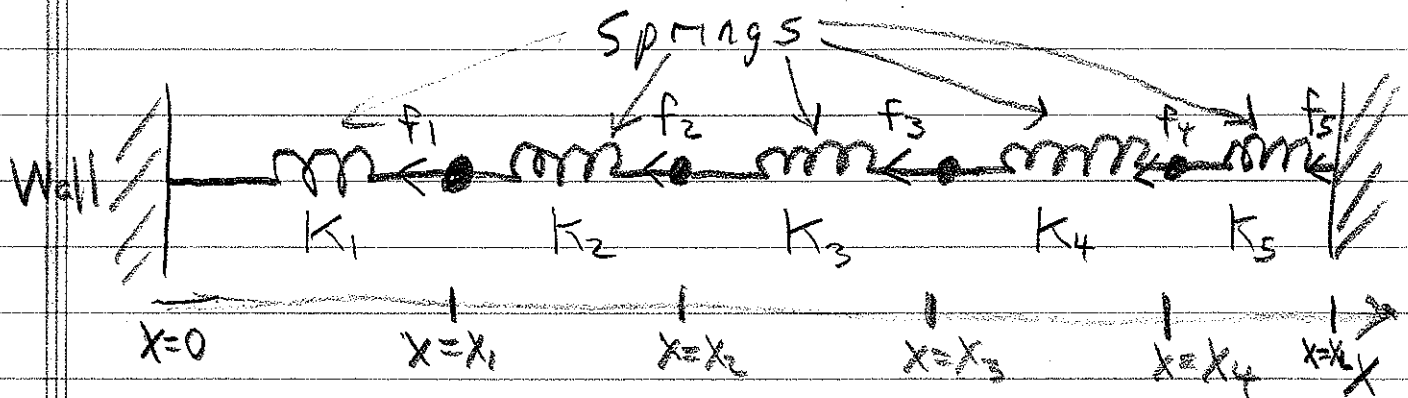

Tight Ideal Spring



$$x_a \approx x_b$$

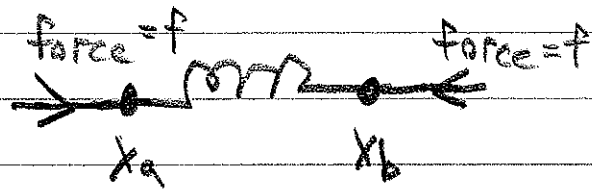

$$f = K_{big} (x_b - x_a)$$

Loose Ideal Spring

$$f = K_{small} (x_b - x_a)$$

Input / Output Approach

Set x_1, x_2, x_3, x_4



Get f_1, f_2, f_3, f_4, f_5

But That's not the question!

What Question is: What are the x 's so that the force balances?

6

Heat Flow

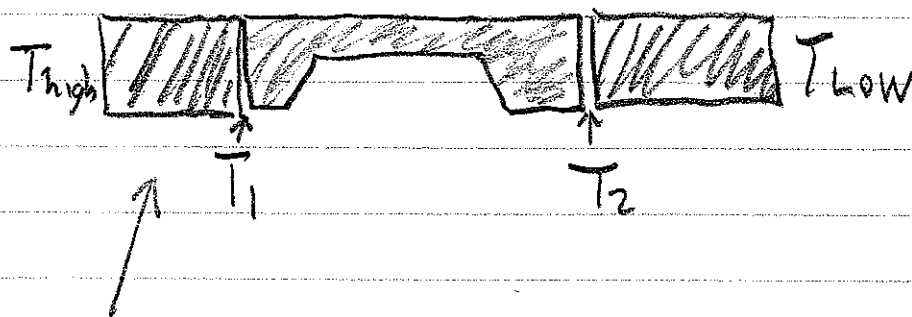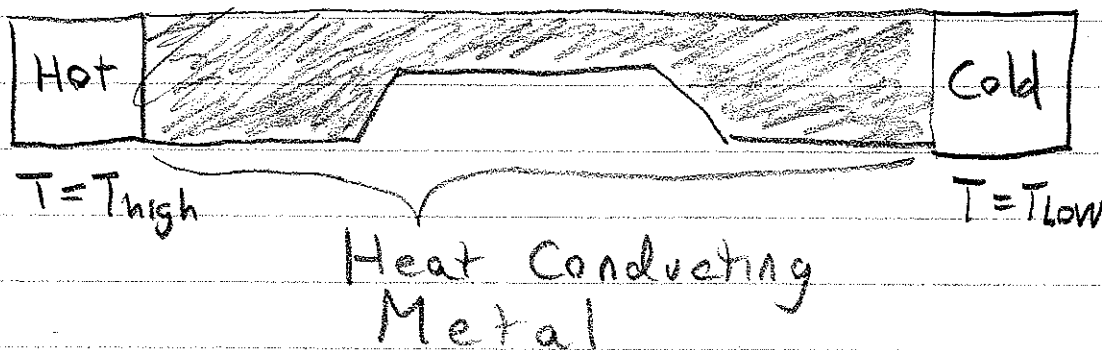

$$\begin{array}{ccc}
 \begin{array}{c} T_{high} \boxed{\text{shaded}} T_1 \\ \xrightarrow{\text{heat flow} = i_{h1}} \\ i_{h1} = K_1(T_{high} - T_1) \end{array} &
 \begin{array}{c} T_1 \boxed{\text{shaded}} T_2 \\ \xrightarrow{i_{h2}} \\ = K_2(T_1 - T_2) \end{array} &
 \begin{array}{c} T_2 \boxed{\text{shaded}} T_{low} \\ \xrightarrow{i_{h3}} \\ = K_3(T_2 - T_{low}) \end{array} \\
 \swarrow \quad \quad \quad \nearrow & & \nearrow \\
 & \text{Thermal conductivities} &
 \end{array}$$

Input / Output Perspective

Set T_1, T_2



Get i_{h1}, i_{h2}, i_{h3}

Not The Right Question!


Right Question { What are T_1 & T_2 so heat flows are Matched?

7

Signal Conduction in a Nerve

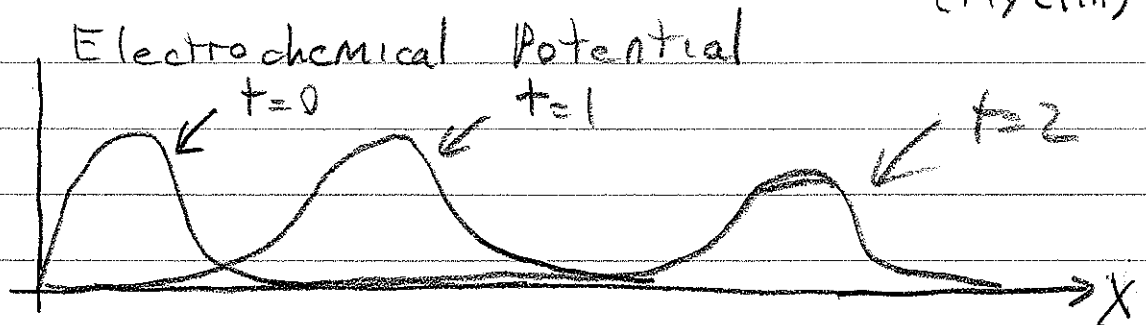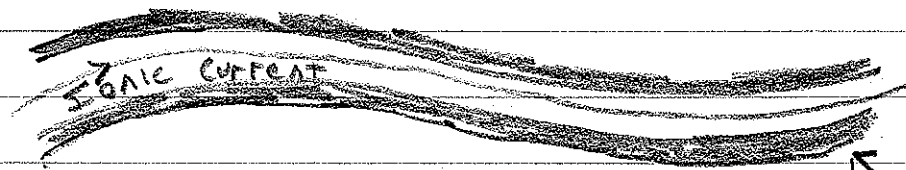

For Multiple Sclerosis

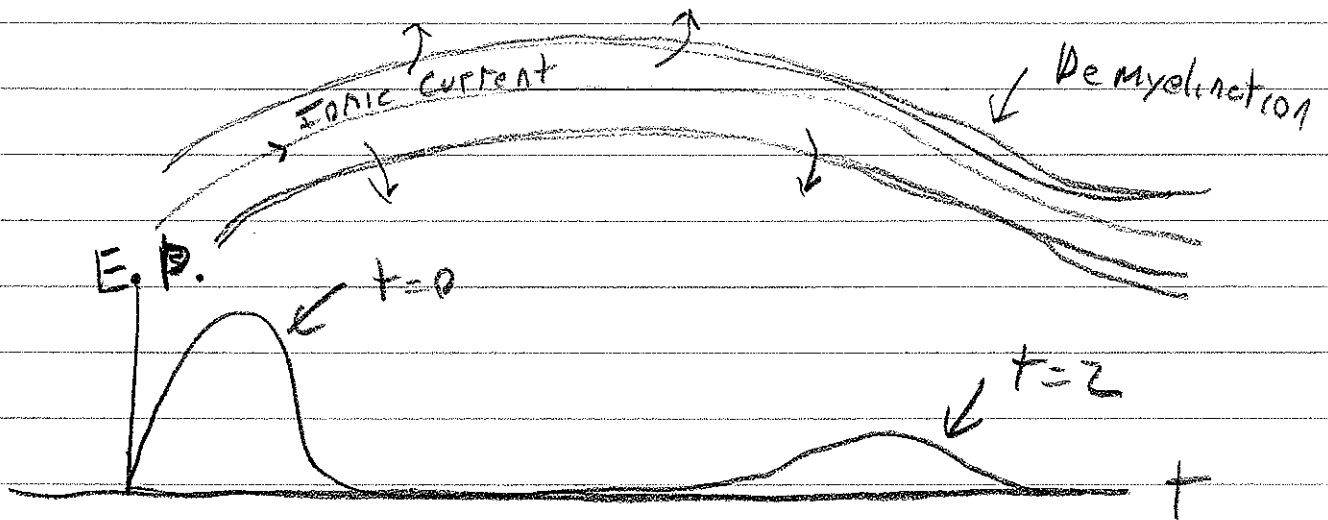

Input / Output Perspective


Set E.P. (x)

Get Ionic Current(x)

Not the right Question!

8


Examples of Constrained Systems

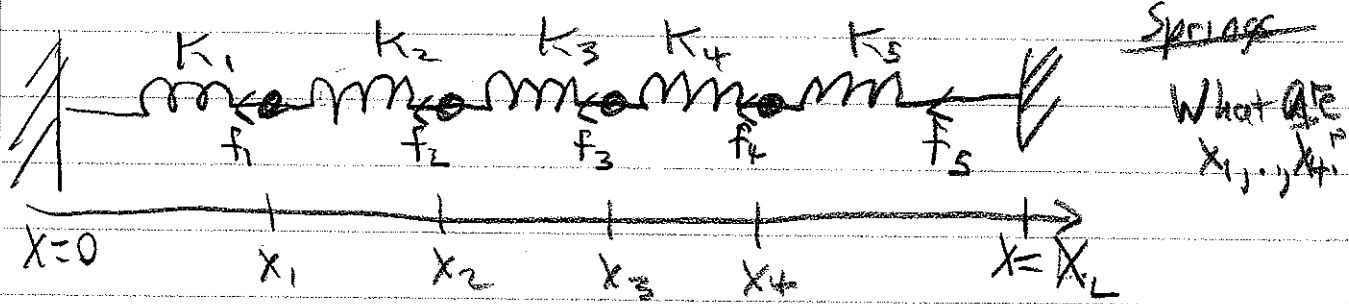

Constitutive Relations $\left\{ \begin{array}{l} K_1(x_1 - 0) = f_1 \\ K_2(x_2 - x_1) = f_2 \\ \dots \\ K_5(x_5 - x_4) = f_5 \end{array} \right.$

Conservation Law $\left\{ \begin{array}{l} f_1 - f_2 = 0 \\ f_2 - f_3 = 0 \\ f_3 - f_4 = 0 \\ f_4 - f_5 = 0 \end{array} \right.$

Force Balance

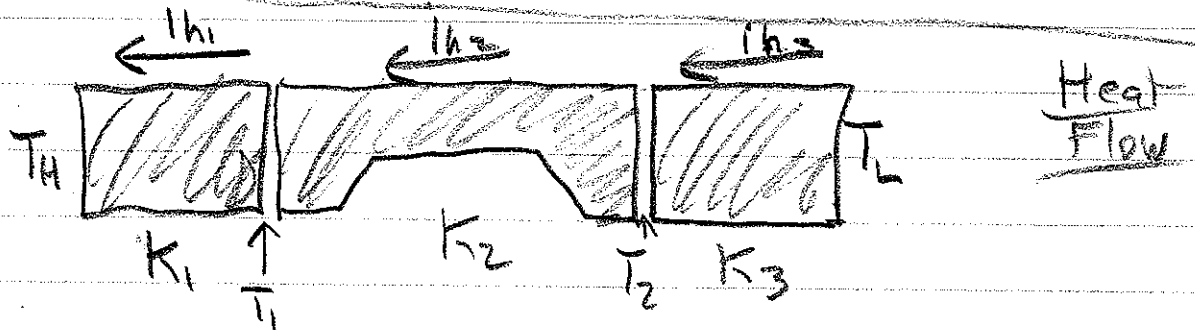


Constitutive Relations $\left\{ \begin{array}{l} K_1(T_1 - T_H) = i_{h1} \\ K_2(T_2 - T_1) = i_{h2} \\ K_3(T_L - T_2) = i_{h3} \end{array} \right.$

Conservation Law $\left\{ \begin{array}{l} i_{h1} - i_{h2} = 0 \\ i_{h2} - i_{h3} = 0 \end{array} \right.$

Heat Flow Balance

Steady-State Nerve Conduction

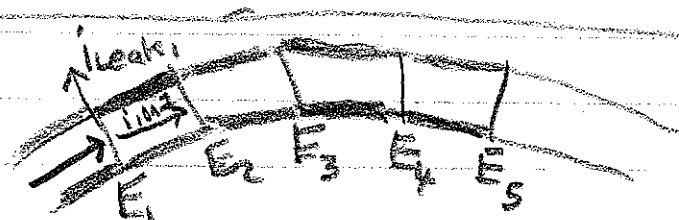

Nerve Conduction

$i_{ionj} = K_j(E_j - E_{j+1}) \quad i_{Leakj} = K_L(E_j)$

$i_{ionj} - i_{ionj-1} + i_{Leakj} = 0$



9

We will study circuits


Variables: Currents, Voltages

Constraints: Constitutive Relations
Element voltage-current relations
Sum of currents at node = 0
Conservation Law
Kirchoff current law (KCL)

Example Constitutive Relations

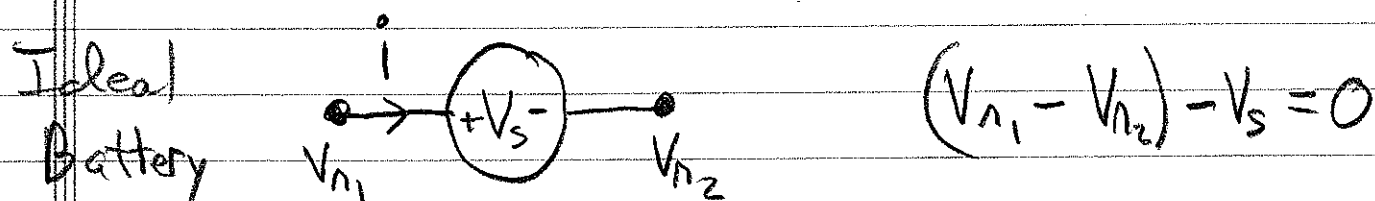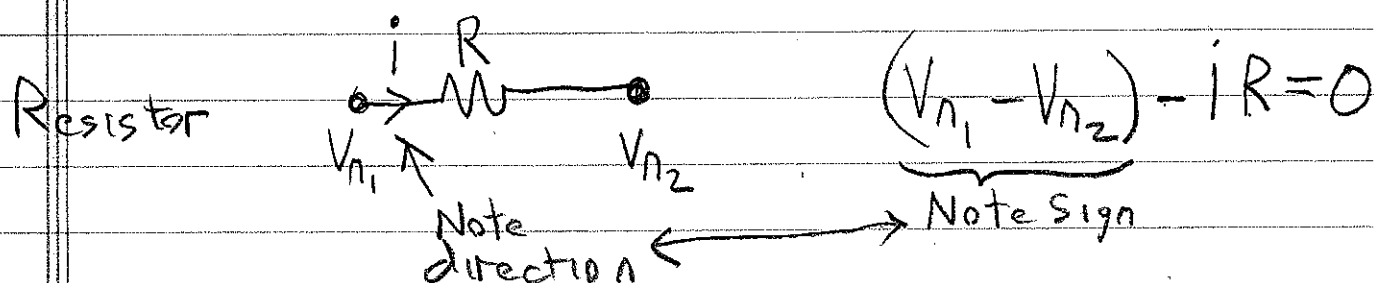

Conservation law

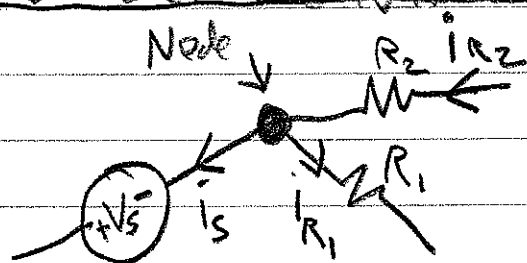

$$\sum_{\text{node}} i's = 0$$

$$i_s + i_{R1} - i_{R2} = 0$$

leaving currents positive


entering current is negative

(10)

Formulating Equations - Nodal Analysis

Circuit

3 unknown
Voltages
5 unknown
currents

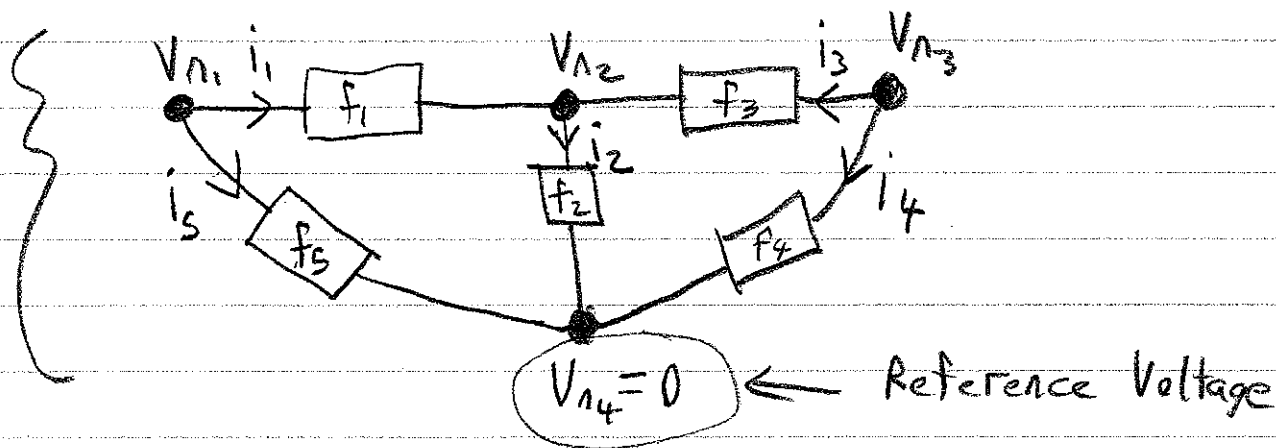

Constitutive Relations

NA Algorithm

5 relations

$$\begin{cases} f_1(i_1, V_{n1}, V_{n2}) = 0 \\ f_2(i_2, V_{n2}, V_{n4}=0) = 0 \\ f_3(i_3, V_{n3}, V_{n2}) = 0 \\ f_4(i_4, V_{n3}, V_{n4}=0) = 0 \\ f_5(i_5, V_{n1}, V_{n4}=0) = 0 \end{cases}$$


- 0) Pick a reference Node
- 1) Label Element Current Arrows
- 2) Write Constitutive relations for each element
- 3) Write Conservation Law for each node (except ref)

Conservation Law

3 relations

$$\begin{cases} i_1 + i_5 = 0 \\ -i_3 + i_2 - i_1 = 0 \\ i_3 + i_4 = 0 \end{cases}$$

(11)

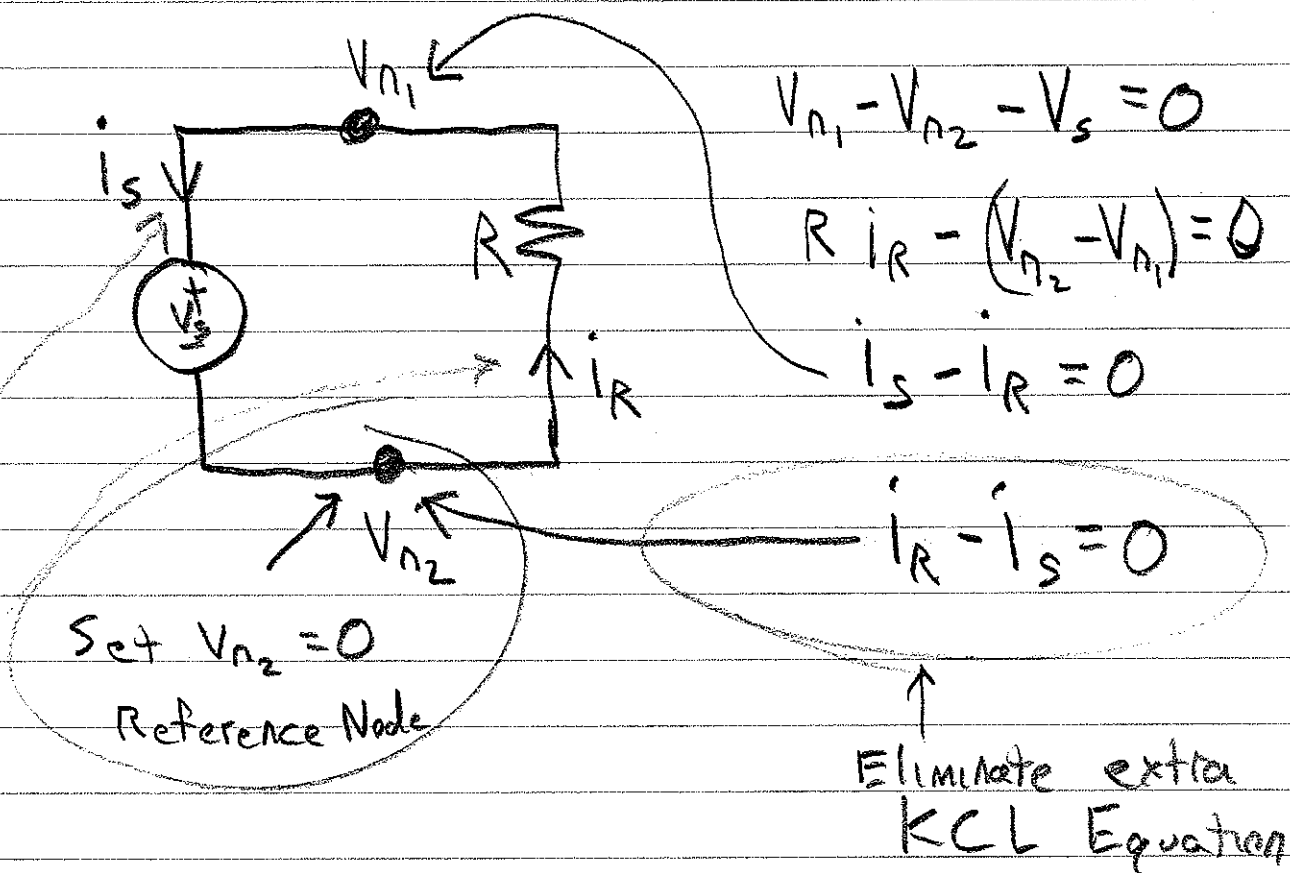Simple Circuit ExampleSolve

$$(V_{n1} - 0) = V_s$$


$$R i_R - (0 - V_{n1}) = 0 = R i_R + V_s$$

Reverse
Directions!

$$i_R = -\frac{V_s}{R}$$

$$i_s = -\frac{V_s}{R}$$

Voltage Divider Example

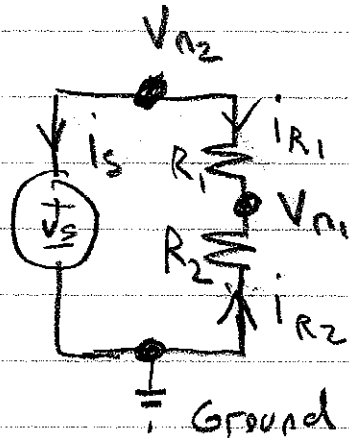Constit

$$(V_{n2} - 0) - V_s = 0$$

$$(V_{n2} - V_{n1}) - R_1 i_{R1} = 0$$

$$(0 - V_{n1}) - R_2 i_{R2} = 0$$

KCL

$$-i_{R1} - i_{R2} = 0$$

$$i_{R1} + i_s = 0$$

Solving

$$\frac{V_s - V_{n1}}{R_1} - i_{R1} + i_{R2} = 0 \Rightarrow \frac{V_s - V_{n1}}{R_1} - \frac{V_{n1}}{R_2} = 0$$


$$(R_1 R_2) \left(+\frac{1}{R_1} + \frac{1}{R_2} \right) V_{n1} = \left(\frac{V_s}{R_1} \right) R_1 R_2$$

$$V_{n1} = V_s \frac{R_2}{R_1 + R_2}$$

Voltage
Divider
Formula

13

Resistors In Series

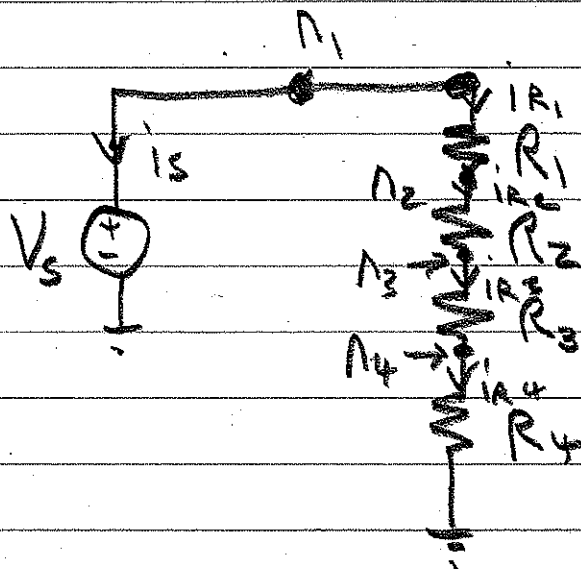

$i_s + i_{R_1} = 0$
 $-i_{R_1} + i_{R_2} = 0$
 $-i_{R_2} + i_{R_3} = 0$
 $-i_{R_3} + i_{R_4} = 0$

KVLs
 Applied
 TWICE

At Gnd
 $-i_s - i_{R_4} = 0$

$V_{n_1} - V_{n_2} - i_{R_1} R_1 = 0$


$V_{n_2} - V_{n_3} - i_{R_2} R_2 = 0$

$V_{n_3} - V_{n_4} - i_{R_3} R_3 = 0$

$V_{n_4} - 0 - i_{R_4} R_4 = 0$


$i_s = -i_{R_1} = -i_{R_2} = -i_{R_3} = -i_{R_4} = -i_T$

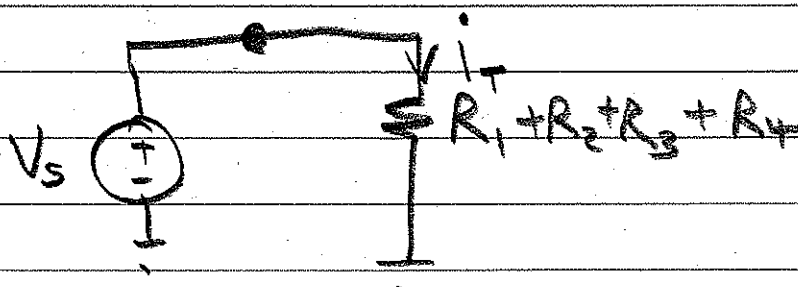$\Rightarrow V_{n_1} - 0 - i_T (R_1 + R_2 + R_3 + R_4) = 0$



Resistors
Add
in Series

Resistor Line

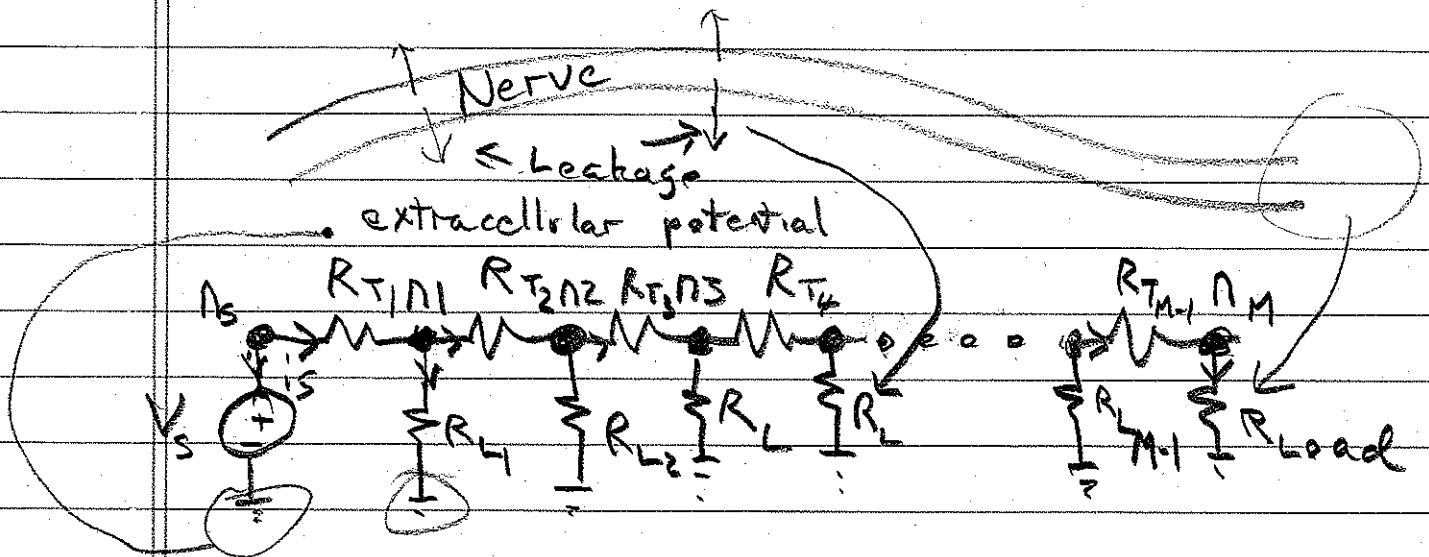

Two
terminal
currents
appear
in
two
KCL
eqns

$$\begin{aligned}
 n_s: \quad i_s + i_{RT_1} &= 0 \\
 n_1: \quad -i_{RT_1} + i_{RT_2} + i_{R_{L1}} &= 0 \\
 n_2: \quad -i_{RT_2} + i_{R_{L2}} + i_{RT_3} &= 0 \\
 &\vdots \\
 n_M: \quad -i_{RT_{M-1}} + i_{R_{Load}} &= 0
 \end{aligned}$$

i_{RT} 's
Appear
twice
 i_{R_L} 's & i_s
appear
once.
Why?

$$V_{AS} - 0 - V_s = 0$$

$$V_{AS} - V_{A1} - i_{RT_1} R_{T1} = 0$$

$$V_{A2} - V_{A1} - i_{RT_2} R_{T2} = 0$$

(15)

Resistor Linc (Cont'd)

KCL For Reference Node


$$\text{Gnd} \quad -i_s - i_{R_1} - i_{R_2} - \dots - i_{R_{L-1}} - i_{R_{\text{load}}} = 0$$

Some Observations

$$\text{Suppose } 1 = R_{T_1} = R_{T_2} = \dots = R_{T_{M-1}} = R_{\text{load}}$$

$$1000 = R_{L_1} = \dots = R_{L_{M-1}}$$
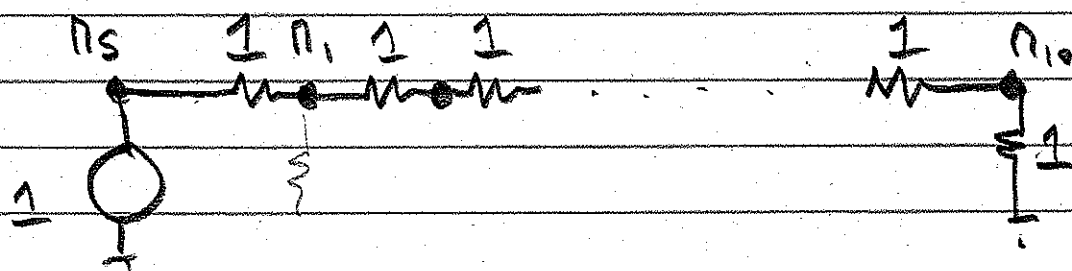
$$\text{If } V_s = 10, \approx \text{ what is } V_{AM}$$



$$\text{If } R_{L_s} = 1, \text{ what is } V_{AM}?$$